

# Chp 30: Inductance - (III)

## Energy in an R-L circuit

When the current in an *R-L* circuit is decaying, what fraction of the original energy stored in the inductor has been dissipated after 2.3 time constants?

## Energy in an R-L circuit

When the current in an *R-L* circuit is decaying, what fraction of the original energy stored in the inductor has been dissipated after 2.3 time constants?

$$i = I_0 e^{-(R/L)t} \quad U = \frac{1}{2} L i^2 \quad \rightarrow \quad U = \frac{1}{2} L I_0^2 e^{-2(R/L)t} = U_0 e^{-2(R/L)t}$$

$U_0 = \frac{1}{2} L I_0^2$  is the energy at the initial time  $t=0$ . When  $t=2.3T=2.3L/R$

## Energy in an R-L circuit

When the current in an *R-L* circuit is decaying, what fraction of the original energy stored in the inductor has been dissipated after 2.3 time constants?

$$i = I_0 e^{-(R/L)t} \quad U = \frac{1}{2} L i^2 \quad \rightarrow \quad U = \frac{1}{2} L I_0^2 e^{-2(R/L)t} = U_0 e^{-2(R/L)t}$$


$U_0 = \frac{1}{2} L I_0^2$  is the energy at the initial time  $t=0$ . When  $t=2.3T=2.3L/R$


$$\rightarrow U = U_0 e^{-2(2.3)} = U_0 e^{-4.6} = 0.010 U_0$$

That is, only 0.010 or 1.0% of the energy initially stored in the inductor remains, so 99.0% has been dissipated in the resistor.

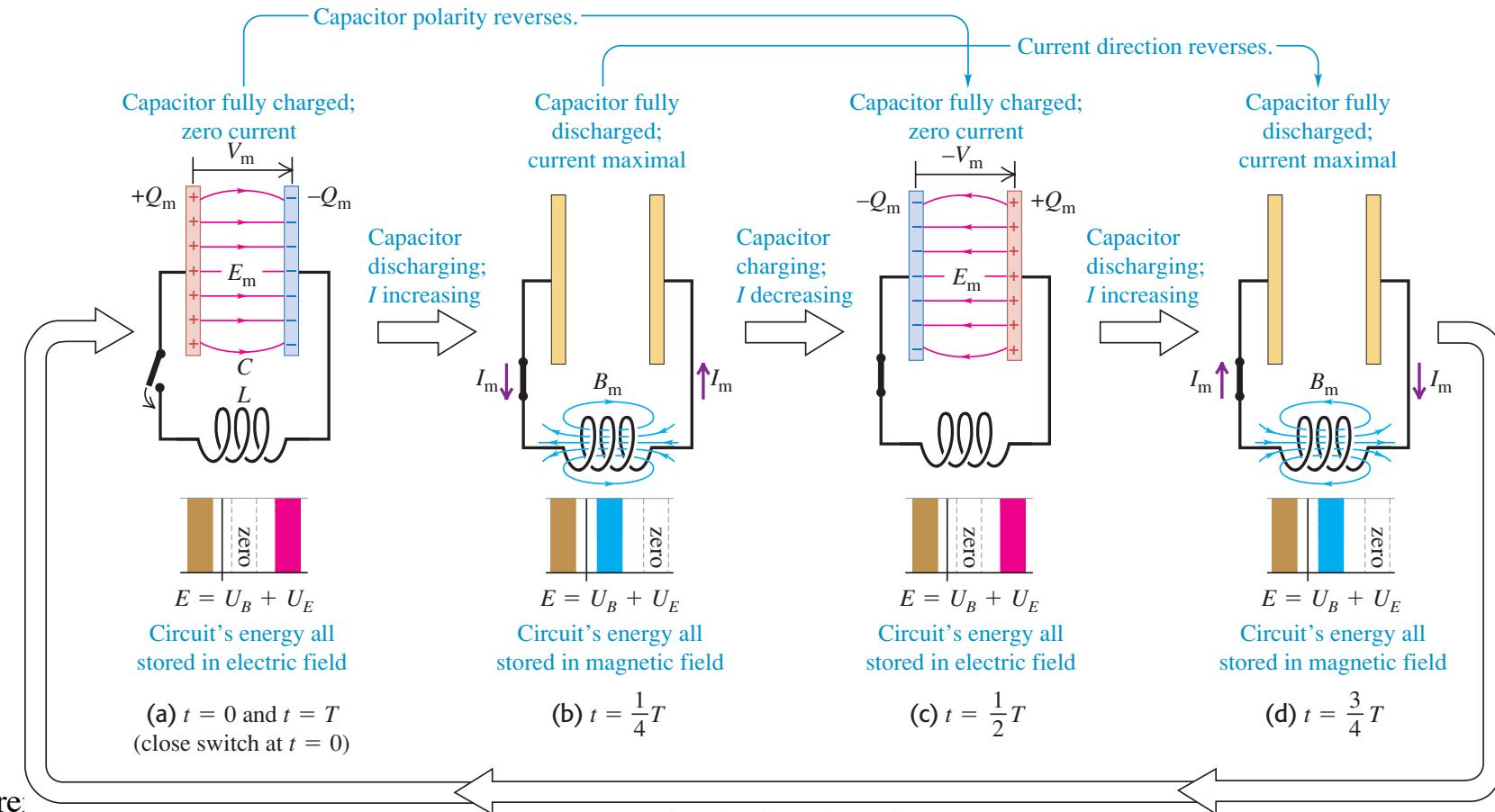
# The L-C Circuit

A circuit containing an inductor and a capacitor shows an entirely new mode of behavior, characterized by *oscillating current and charge*. This is in sharp contrast to the *exponential approach* to a steady-state situation that we have seen with both *R-C* and *R-L* circuits. In the *L-C* circuit we charge the capacitor to a potential difference  $V_m$  and initial charge  $Q = CV_m$  on its left-hand plate and then close the switch. The capacitor begins to discharge through the inductor. Because of the induced emf in the inductor, the current cannot change instantaneously it starts at zero and eventually builds up to a maximum value  $I_m$ . During this buildup the capacitor is discharging  $\rightarrow$  *electrical oscillation*




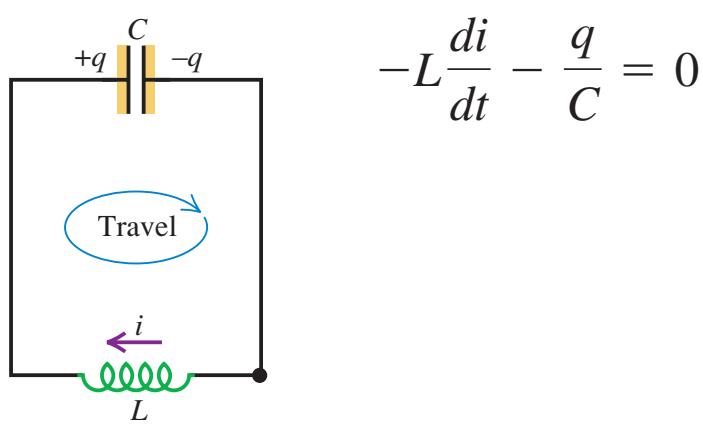

$$-L \frac{di}{dt} - \frac{q}{C} = 0$$

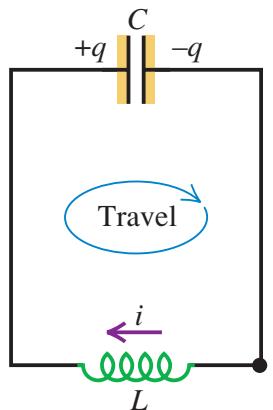

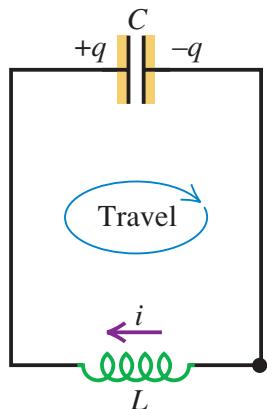
$$-L \frac{di}{dt} - \frac{q}{C} = 0 \quad \Rightarrow \quad \frac{d^2q}{dt^2} + \frac{1}{LC}q = 0$$



$$-L \frac{di}{dt} - \frac{q}{C} = 0 \quad \Rightarrow \quad \frac{d^2q}{dt^2} + \frac{1}{LC}q = 0$$

Similar to the equation we derived for simple harmonic motion

$$\frac{d^2x}{dt^2} + \frac{k}{m}x = 0$$

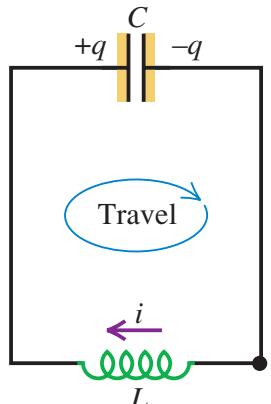

$$-L \frac{di}{dt} - \frac{q}{C} = 0 \quad \Rightarrow \quad \frac{d^2q}{dt^2} + \frac{1}{LC}q = 0$$


Similar to the equation we derived for simple harmonic motion

$$\frac{d^2x}{dt^2} + \frac{k}{m}x = 0$$

$$x = A \cos(\omega t + \phi) \quad \Leftrightarrow \quad q = Q \cos(\omega t + \phi)$$

$$\omega = \sqrt{\frac{1}{LC}}$$

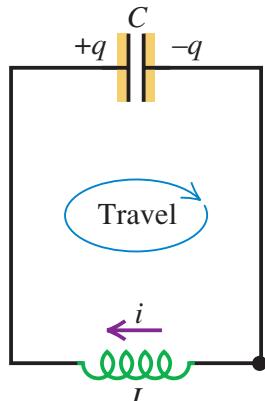angular frequency of oscillation in an  $L-C$  circuit



$$-L \frac{di}{dt} - \frac{q}{C} = 0 \quad \Rightarrow \quad \frac{d^2q}{dt^2} + \frac{1}{LC}q = 0$$

Similar to the equation we derived for simple harmonic motion


$$\frac{d^2x}{dt^2} + \frac{k}{m}x = 0$$

$$x = A \cos(\omega t + \phi) \quad \Leftrightarrow \quad q = Q \cos(\omega t + \phi)$$

$$\omega = \sqrt{\frac{1}{LC}}$$

$$i = dq/dt \quad \Rightarrow \quad i = -\omega Q \sin(\omega t + \phi) \quad \omega = 2\pi f$$

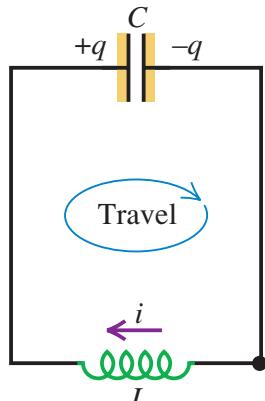angular frequency of oscillation in an  $L-C$  circuit



$$-L \frac{di}{dt} - \frac{q}{C} = 0 \quad \Rightarrow \quad \frac{d^2q}{dt^2} + \frac{1}{LC}q = 0$$

Similar to the equation we derived for simple harmonic motion

$$\frac{d^2x}{dt^2} + \frac{k}{m}x = 0$$

$$x = A \cos(\omega t + \phi) \quad \Leftrightarrow \quad q = Q \cos(\omega t + \phi)$$

$$\omega = \sqrt{\frac{1}{LC}}$$

$$i = dq/dt \quad \Rightarrow \quad i = -\omega Q \sin(\omega t + \phi)$$

$$\omega = 2\pi f$$

angular frequency of oscillation in an  $L-C$  circuit

## Mass-Spring System

$$\text{Kinetic energy} = \frac{1}{2}mv_x^2$$

$$\text{Potential energy} = \frac{1}{2}kx^2$$

$$\frac{1}{2}mv_x^2 + \frac{1}{2}kx^2 = \frac{1}{2}kA^2$$

$$v_x = \pm \sqrt{k/m} \sqrt{A^2 - x^2}$$

$$v_x = dx/dt$$

$$\omega = \sqrt{\frac{k}{m}}$$

$$x = A \cos(\omega t + \phi)$$

## Inductor-Capacitor Circuit

$$\text{Magnetic energy} = \frac{1}{2}Li^2$$

$$\text{Electric energy} = q^2/2C$$

$$\frac{1}{2}Li^2 + q^2/2C = Q^2/2C$$

$$i = \pm \sqrt{1/LC} \sqrt{Q^2 - q^2}$$

$$i = dq/dt$$

$$\omega = \sqrt{\frac{1}{LC}}$$

$$q = Q \cos(\omega t + \phi)$$

## An oscillating circuit

A 300-V dc power supply is used to charge a  $25\text{-}\mu\text{F}$  capacitor. After the capacitor is fully charged, it is disconnected from the power supply and connected across a  $10\text{-mH}$  inductor. The resistance in the circuit is negligible. Find

- (a) the frequency and period of oscillation of the circuit.
- (b) the capacitor charge and the circuit current 1.2 ms after the inductor and capacitor are connected.

# An oscillating circuit

A 300-V dc power supply is used to charge a  $25\text{-}\mu\text{F}$  capacitor. After the capacitor is fully charged, it is disconnected from the power supply and connected across a  $10\text{-mH}$  inductor. The resistance in the circuit is negligible. Find

- the frequency and period of oscillation of the circuit.
- the capacitor charge and the circuit current 1.2 ms after the inductor and capacitor are connected.

$$\omega = \sqrt{\frac{1}{LC}} \quad \omega = 2\pi f \quad q = Q \cos(\omega t + \phi) \quad i = -\omega Q \sin(\omega t + \phi)$$

# An oscillating circuit

A 300-V dc power supply is used to charge a  $25\text{-}\mu\text{F}$  capacitor. After the capacitor is fully charged, it is disconnected from the power supply and connected across a  $10\text{-mH}$  inductor. The resistance in the circuit is negligible. Find

- the frequency and period of oscillation of the circuit.
- the capacitor charge and the circuit current 1.2 ms after the inductor and capacitor are connected.

$$\omega = \sqrt{\frac{1}{LC}} \quad \omega = 2\pi f \quad q = Q \cos(\omega t + \phi) \quad i = -\omega Q \sin(\omega t + \phi)$$

Initially the capacitor is fully charged and the current is zero, so the phase angle is  $\phi = 0$


$$\omega = \sqrt{\frac{1}{(10 \times 10^{-3} \text{ H})(25 \times 10^{-6} \text{ F})}} = 2.0 \times 10^3 \text{ rad/s}$$

# An oscillating circuit

A 300-V dc power supply is used to charge a  $25\text{-}\mu\text{F}$  capacitor. After the capacitor is fully charged, it is disconnected from the power supply and connected across a  $10\text{-mH}$  inductor. The resistance in the circuit is negligible. Find

- the frequency and period of oscillation of the circuit.
- the capacitor charge and the circuit current 1.2 ms after the inductor and capacitor are connected.

$$\omega = \sqrt{\frac{1}{LC}} \quad \omega = 2\pi f \quad q = Q \cos(\omega t + \phi) \quad i = -\omega Q \sin(\omega t + \phi)$$

Initially the capacitor is fully charged and the current is zero, so the phase angle is  $\phi = 0$

$$\rightarrow \omega = \sqrt{\frac{1}{(10 \times 10^{-3} \text{ H})(25 \times 10^{-6} \text{ F})}} = 2.0 \times 10^3 \text{ rad/s}$$

$$\rightarrow f = \frac{\omega}{2\pi} = \frac{2.0 \times 10^3 \text{ rad/s}}{2\pi \text{ rad/cycle}} = 320 \text{ Hz} \quad T = \frac{1}{f} = \frac{1}{320 \text{ Hz}} = 3.1 \times 10^{-3} \text{ s} = 3.1 \text{ ms}$$

# An oscillating circuit

A 300-V dc power supply is used to charge a  $25\text{-}\mu\text{F}$  capacitor. After the capacitor is fully charged, it is disconnected from the power supply and connected across a  $10\text{-mH}$  inductor. The resistance in the circuit is negligible. Find

(a) the frequency and period of oscillation of the circuit.

(b) the capacitor charge and the circuit current 1.2 ms after the inductor and capacitor are connected.

$$\omega = \sqrt{\frac{1}{LC}} \quad \omega = 2\pi f \quad q = Q \cos(\omega t + \phi) \quad i = -\omega Q \sin(\omega t + \phi)$$

Initially the capacitor is fully charged and the current is zero, so the phase angle is  $\phi = 0$

$$\rightarrow \omega = \sqrt{\frac{1}{(10 \times 10^{-3} \text{ H})(25 \times 10^{-6} \text{ F})}} = 2.0 \times 10^3 \text{ rad/s}$$

$$\rightarrow f = \frac{\omega}{2\pi} = \frac{2.0 \times 10^3 \text{ rad/s}}{2\pi \text{ rad/cycle}} = 320 \text{ Hz} \quad T = \frac{1}{f} = \frac{1}{320 \text{ Hz}} = 3.1 \times 10^{-3} \text{ s} = 3.1 \text{ ms}$$

The charge is maximum at  $t = 0$ , so  $\phi = 0$  and  $Q = CE = (25 \times 10^{-6} \text{ F})(300 \text{ V}) = 7.5 \times 10^{-3} \text{ C}$

# An oscillating circuit

A 300-V dc power supply is used to charge a  $25\text{-}\mu\text{F}$  capacitor. After the capacitor is fully charged, it is disconnected from the power supply and connected across a  $10\text{-mH}$  inductor. The resistance in the circuit is negligible. Find

(a) the frequency and period of oscillation of the circuit.

(b) the capacitor charge and the circuit current 1.2 ms after the inductor and capacitor are connected.

$$\omega = \sqrt{\frac{1}{LC}} \quad \omega = 2\pi f \quad q = Q \cos(\omega t + \phi) \quad i = -\omega Q \sin(\omega t + \phi)$$

Initially the capacitor is fully charged and the current is zero, so the phase angle is  $\phi = 0$

$$\rightarrow \omega = \sqrt{\frac{1}{(10 \times 10^{-3} \text{ H})(25 \times 10^{-6} \text{ F})}} = 2.0 \times 10^3 \text{ rad/s}$$

$$\rightarrow f = \frac{\omega}{2\pi} = \frac{2.0 \times 10^3 \text{ rad/s}}{2\pi \text{ rad/cycle}} = 320 \text{ Hz} \quad T = \frac{1}{f} = \frac{1}{320 \text{ Hz}} = 3.1 \times 10^{-3} \text{ s} = 3.1 \text{ ms}$$

The charge is maximum at  $t = 0$ , so  $\phi = 0$  and  $Q = CE = (25 \times 10^{-6} \text{ F})(300 \text{ V}) = 7.5 \times 10^{-3} \text{ C}$

$$\rightarrow q = (7.5 \times 10^{-3} \text{ C}) \cos \omega t$$

# An oscillating circuit

A 300-V dc power supply is used to charge a  $25\text{-}\mu\text{F}$  capacitor. After the capacitor is fully charged, it is disconnected from the power supply and connected across a  $10\text{-mH}$  inductor. The resistance in the circuit is negligible. Find

(a) the frequency and period of oscillation of the circuit.

(b) the capacitor charge and the circuit current 1.2 ms after the inductor and capacitor are connected.

$$\omega = \sqrt{\frac{1}{LC}} \quad \omega = 2\pi f \quad q = Q \cos(\omega t + \phi) \quad i = -\omega Q \sin(\omega t + \phi)$$

Initially the capacitor is fully charged and the current is zero, so the phase angle is  $\phi = 0$

$$\rightarrow \omega = \sqrt{\frac{1}{(10 \times 10^{-3} \text{ H})(25 \times 10^{-6} \text{ F})}} = 2.0 \times 10^3 \text{ rad/s}$$

$$\rightarrow f = \frac{\omega}{2\pi} = \frac{2.0 \times 10^3 \text{ rad/s}}{2\pi \text{ rad/cycle}} = 320 \text{ Hz} \quad T = \frac{1}{f} = \frac{1}{320 \text{ Hz}} = 3.1 \times 10^{-3} \text{ s} = 3.1 \text{ ms}$$

The charge is maximum at  $t = 0$ , so  $\phi = 0$  and  $Q = CE = (25 \times 10^{-6} \text{ F})(300 \text{ V}) = 7.5 \times 10^{-3} \text{ C}$

$$\rightarrow q = (7.5 \times 10^{-3} \text{ C}) \cos \omega t$$

At time  $t = 1.2 \times 10^{-3} \text{ s} \rightarrow \omega t = (2.0 \times 10^3 \text{ rad/s})(1.2 \times 10^{-3} \text{ s}) = 2.4 \text{ rad}$

# An oscillating circuit

A 300-V dc power supply is used to charge a  $25\text{-}\mu\text{F}$  capacitor. After the capacitor is fully charged, it is disconnected from the power supply and connected across a  $10\text{-mH}$  inductor. The resistance in the circuit is negligible. Find

(a) the frequency and period of oscillation of the circuit.

(b) the capacitor charge and the circuit current 1.2 ms after the inductor and capacitor are connected.

$$\omega = \sqrt{\frac{1}{LC}} \quad \omega = 2\pi f \quad q = Q \cos(\omega t + \phi) \quad i = -\omega Q \sin(\omega t + \phi)$$

Initially the capacitor is fully charged and the current is zero, so the phase angle is  $\phi = 0$

$$\rightarrow \omega = \sqrt{\frac{1}{(10 \times 10^{-3} \text{ H})(25 \times 10^{-6} \text{ F})}} = 2.0 \times 10^3 \text{ rad/s}$$

$$\rightarrow f = \frac{\omega}{2\pi} = \frac{2.0 \times 10^3 \text{ rad/s}}{2\pi \text{ rad/cycle}} = 320 \text{ Hz} \quad T = \frac{1}{f} = \frac{1}{320 \text{ Hz}} = 3.1 \times 10^{-3} \text{ s} = 3.1 \text{ ms}$$

The charge is maximum at  $t = 0$ , so  $\phi = 0$  and  $Q = CE = (25 \times 10^{-6} \text{ F})(300 \text{ V}) = 7.5 \times 10^{-3} \text{ C}$

$$\rightarrow q = (7.5 \times 10^{-3} \text{ C}) \cos \omega t$$

At time  $t = 1.2 \times 10^{-3} \text{ s} \rightarrow \omega t = (2.0 \times 10^3 \text{ rad/s})(1.2 \times 10^{-3} \text{ s}) = 2.4 \text{ rad}$

$$\rightarrow q = (7.5 \times 10^{-3} \text{ C}) \cos(2.4 \text{ rad}) = -5.5 \times 10^{-3} \text{ C}$$

# An oscillating circuit

A 300-V dc power supply is used to charge a  $25\text{-}\mu\text{F}$  capacitor. After the capacitor is fully charged, it is disconnected from the power supply and connected across a  $10\text{-mH}$  inductor. The resistance in the circuit is negligible. Find

(a) the frequency and period of oscillation of the circuit.

(b) the capacitor charge and the circuit current 1.2 ms after the inductor and capacitor are connected.

$$\omega = \sqrt{\frac{1}{LC}} \quad \omega = 2\pi f \quad q = Q \cos(\omega t + \phi) \quad i = -\omega Q \sin(\omega t + \phi)$$

Initially the capacitor is fully charged and the current is zero, so the phase angle is  $\phi = 0$

$$\rightarrow \omega = \sqrt{\frac{1}{(10 \times 10^{-3} \text{ H})(25 \times 10^{-6} \text{ F})}} = 2.0 \times 10^3 \text{ rad/s}$$

$$\rightarrow f = \frac{\omega}{2\pi} = \frac{2.0 \times 10^3 \text{ rad/s}}{2\pi \text{ rad/cycle}} = 320 \text{ Hz} \quad T = \frac{1}{f} = \frac{1}{320 \text{ Hz}} = 3.1 \times 10^{-3} \text{ s} = 3.1 \text{ ms}$$

The charge is maximum at  $t = 0$ , so  $\phi = 0$  and  $Q = CE = (25 \times 10^{-6} \text{ F})(300 \text{ V}) = 7.5 \times 10^{-3} \text{ C}$

$$\rightarrow q = (7.5 \times 10^{-3} \text{ C}) \cos \omega t$$

At time  $t = 1.2 \times 10^{-3} \text{ s} \rightarrow \omega t = (2.0 \times 10^3 \text{ rad/s})(1.2 \times 10^{-3} \text{ s}) = 2.4 \text{ rad}$

$$\rightarrow q = (7.5 \times 10^{-3} \text{ C}) \cos(2.4 \text{ rad}) = -5.5 \times 10^{-3} \text{ C}$$

$$i = -(2.0 \times 10^3 \text{ rad/s})(7.5 \times 10^{-3} \text{ C}) \sin(2.4 \text{ rad}) = -10 \text{ A}$$

## Energy in an oscillating circuit

For the previous L-C circuit. Find magnetic and electrical energies at

- (a)  $t = 0$
- (b)  $t = 1.2 \text{ ms}$ .

## Energy in an oscillating circuit

For the previous L-C circuit. Find magnetic and electrical energies at

(a)  $t = 0$

(b)  $t = 1.2 \text{ ms}$ .

We must calculate the magnetic energy  $U_B$  (stored in the inductor) and the electric energy  $U_E$  (stored in the capacitor) at two times during the L-C circuit oscillation.

$$U_B = \frac{1}{2}Li^2 \quad U_E = q^2/2C$$

(a) At  $t=0 \rightarrow i=0$        $U_B = \frac{1}{2}Li^2 = 0$        $U_E = \frac{Q^2}{2C} = \frac{(7.5 \times 10^{-3} \text{ C})^2}{2(25 \times 10^{-6} \text{ F})} = 1.1 \text{ J}$

# Energy in an oscillating circuit

For the previous L-C circuit. Find magnetic and electrical energies at

(a)  $t = 0$

(b)  $t = 1.2 \text{ ms}$ .

We must calculate the magnetic energy  $U_B$  (stored in the inductor) and the electric energy  $U_E$  (stored in the capacitor) at two times during the L-C circuit oscillation.

$$U_B = \frac{1}{2}Li^2 \quad U_E = q^2/2C$$

(a) At  $t=0 \rightarrow i=0$        $U_B = \frac{1}{2}Li^2 = 0$        $U_E = \frac{Q^2}{2C} = \frac{(7.5 \times 10^{-3} \text{ C})^2}{2(25 \times 10^{-6} \text{ F})} = 1.1 \text{ J}$

(a) At  $t=1.2 \text{ ms} \rightarrow$  we have found  $i=10 \text{ A}$  and  $q=-5.5 \times 10^{-3} \text{ C}$

$$U_B = \frac{1}{2}Li^2 = \frac{1}{2}(10 \times 10^{-3} \text{ H})(-10 \text{ A})^2 = 0.5 \text{ J}$$

→       $U_E = \frac{q^2}{2C} = \frac{(-5.5 \times 10^{-3} \text{ C})^2}{2(25 \times 10^{-6} \text{ F})} = 0.6 \text{ J}$

# Energy in an oscillating circuit

For the previous L-C circuit. Find magnetic and electrical energies at

(a)  $t = 0$

(b)  $t = 1.2 \text{ ms}$ .

We must calculate the magnetic energy  $U_B$  (stored in the inductor) and the electric energy  $U_E$  (stored in the capacitor) at two times during the L-C circuit oscillation.

$$U_B = \frac{1}{2}Li^2 \quad U_E = q^2/2C$$

(a) At  $t=0 \rightarrow i=0$        $U_B = \frac{1}{2}Li^2 = 0$        $U_E = \frac{Q^2}{2C} = \frac{(7.5 \times 10^{-3} \text{ C})^2}{2(25 \times 10^{-6} \text{ F})} = 1.1 \text{ J}$

(a) At  $t=1.2 \text{ ms} \rightarrow$  we have found  $i=10 \text{ A}$  and  $q=-5.5 \times 10^{-3} \text{ C}$

$$\begin{aligned} U_B &= \frac{1}{2}Li^2 = \frac{1}{2}(10 \times 10^{-3} \text{ H})(-10 \text{ A})^2 = 0.5 \text{ J} \\ \rightarrow \quad U_E &= \frac{q^2}{2C} = \frac{(-5.5 \times 10^{-3} \text{ C})^2}{2(25 \times 10^{-6} \text{ F})} = 0.6 \text{ J} \end{aligned}$$

The magnetic and electric energies are the same at  $t = 3T/8 = 0.375T$ .


We saw that the time considered in part (b),  $t = 1.2 \text{ ms}$ , equals  $0.38T$ ; this is slightly later than  $0.375T$ , so  $U_B$  is slightly less than  $U_E$ .

At all times the total energy  $E = U_B + U_E$  has the same value, 1.1 J.

An L-C circuit without resistance is a conservative system; no energy is dissipated.
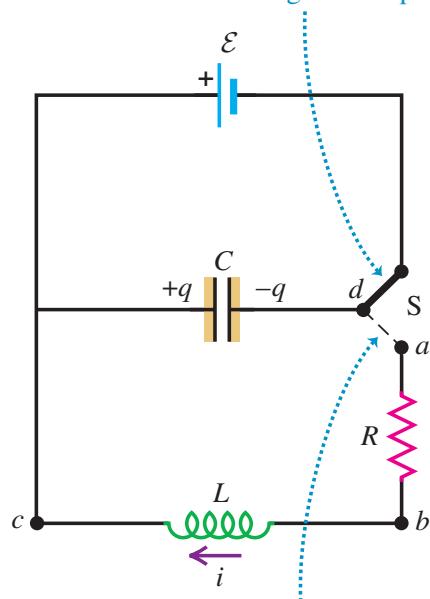
# The $L-R-C$ series circuit


When switch S is in this position,  
the emf charges the capacitor.



When switch S is moved to this  
position, the capacitor discharges  
through the resistor and inductor.
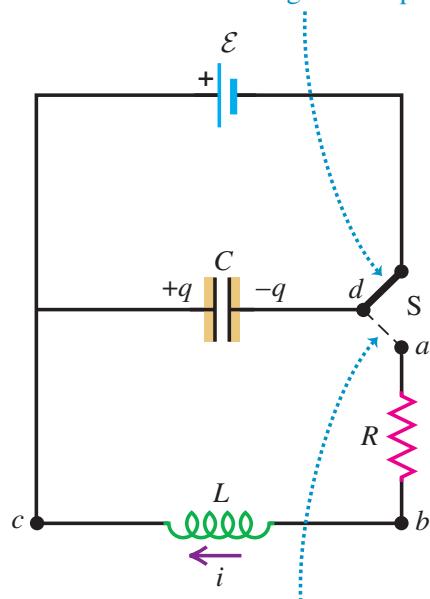
# The $L$ - $R$ - $C$ series circuit

When switch S is in this position, the emf charges the capacitor.




When switch S is moved to this position, the capacitor discharges through the resistor and inductor.

As before, the capacitor starts to discharge as soon as the circuit is completed. But because of  $IR$  losses in the resistor, the magnetic-field energy acquired by the inductor when the capacitor is completely discharged is less than the original electric-field energy of the capacitor. In the same way, the energy of the capacitor when the magnetic field has decreased to zero is still smaller, and so on.
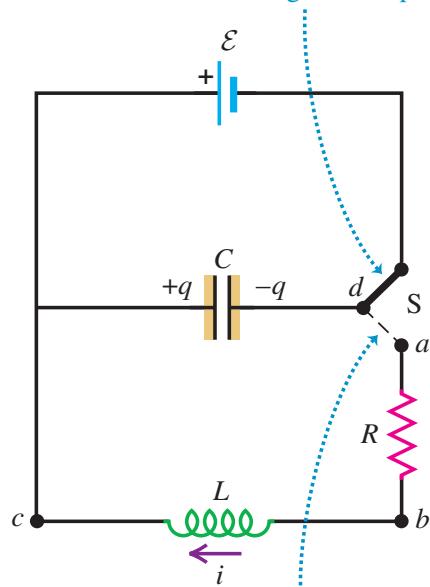
# The $L$ - $R$ - $C$ series circuit

When switch S is in this position,  
the emf charges the capacitor.




When switch S is moved to this  
position, the capacitor discharges  
through the resistor and inductor.


$$-iR - L \frac{di}{dt} - \frac{q}{C} = 0$$

As before, the capacitor starts to discharge as soon as the circuit is completed. But because of  $R^2$  losses in the resistor, the magnetic-field energy acquired by the inductor when the capacitor is completely discharged is less than the original electric-field energy of the capacitor. In the same way, the energy of the capacitor when the magnetic field has decreased to zero is still smaller, and so on.

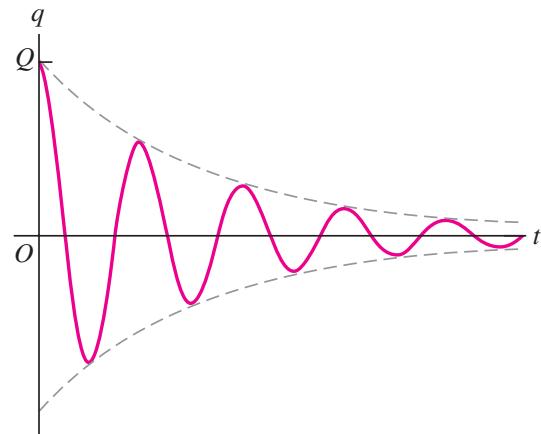(a) Underdamped circuit (small resistance  $R$ )




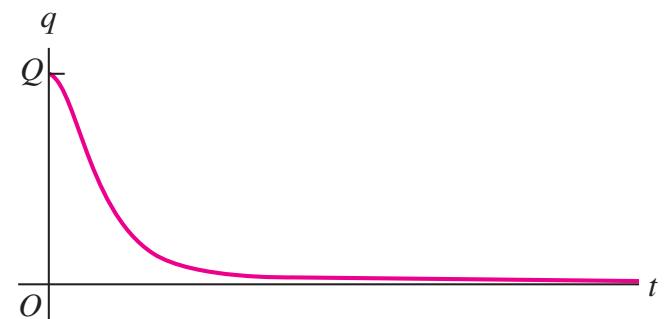(b) Critically damped circuit (larger resistance  $R$ )


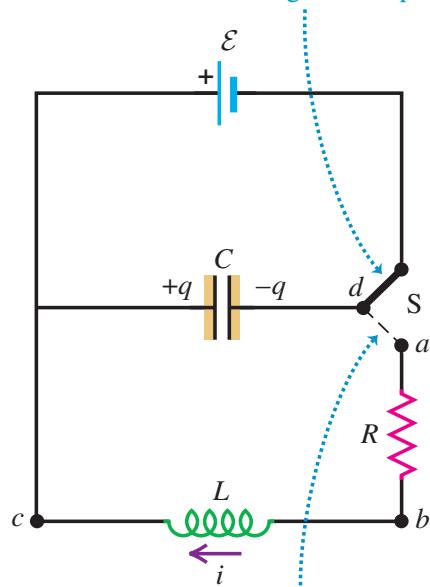
# The $L$ - $R$ - $C$ series circuit

When switch S is in this position, the emf charges the capacitor.



When switch S is moved to this position, the capacitor discharges through the resistor and inductor.


$$-iR - L \frac{di}{dt} - \frac{q}{C} = 0$$




$$\frac{d^2q}{dt^2} + \frac{R}{L} \frac{dq}{dt} + \frac{1}{LC} q = 0$$

As before, the capacitor starts to discharge as soon as the circuit is completed. But because of  $\cancel{R}$  losses in the **resistor**, the magnetic-field energy acquired by the inductor when the capacitor is completely discharged is *less* than the original electric-field energy of the capacitor. In the same way, the energy of the capacitor when the magnetic field has decreased to zero is still smaller, and so on.

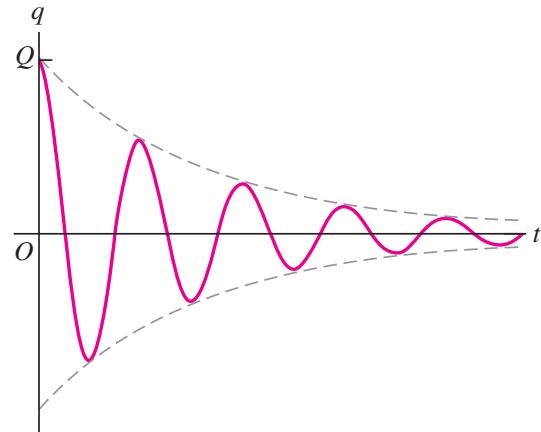(a) Underdamped circuit (small resistance  $R$ )



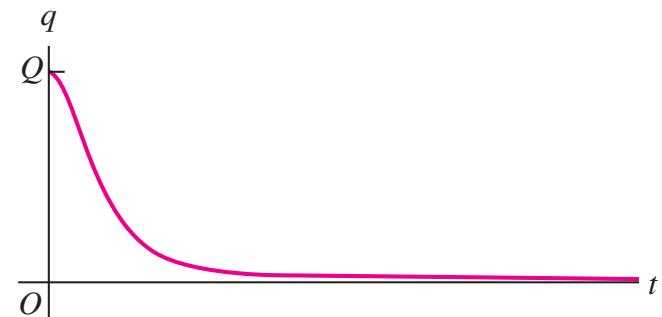
(b) Critically damped circuit (larger resistance  $R$ )



$$q = A e^{-(R/2L)t} \cos\left(\sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}t + \phi\right)$$
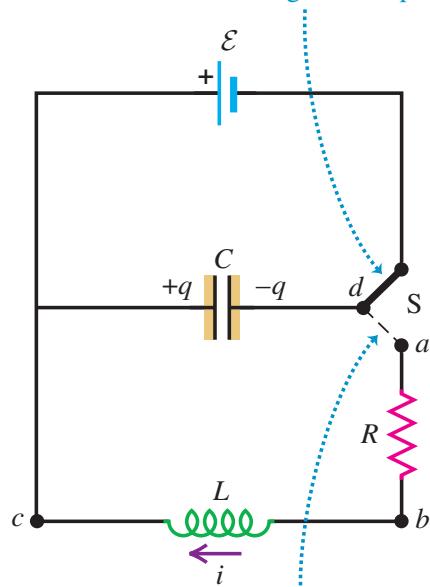
# The $L$ - $R$ - $C$ series circuit

When switch S is in this position,  
the emf charges the capacitor.




When switch S is moved to this  
position, the capacitor discharges  
through the resistor and inductor.

$$-iR - L \frac{di}{dt} - \frac{q}{C} = 0$$


→ 
$$\frac{d^2q}{dt^2} + \frac{R}{L} \frac{dq}{dt} + \frac{1}{LC} q = 0$$

As before, the capacitor starts to discharge as soon as the circuit is completed. But because of  $\cancel{R}$  losses in the **resistor**, the magnetic-field energy acquired by the inductor when the capacitor is completely discharged is *less* than the original electric-field energy of the capacitor. In the same way, the energy of the capacitor when the magnetic field has decreased to zero is still smaller, and so on.

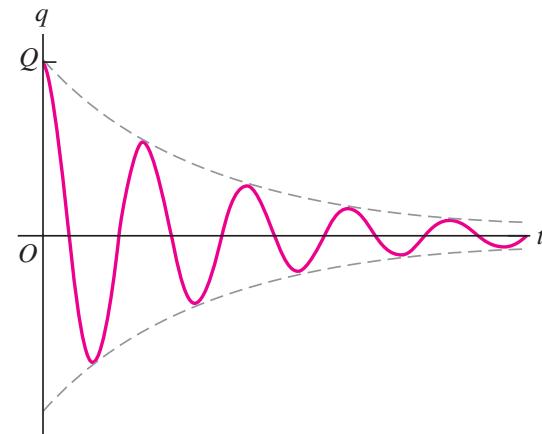(a) Underdamped circuit (small resistance  $R$ )



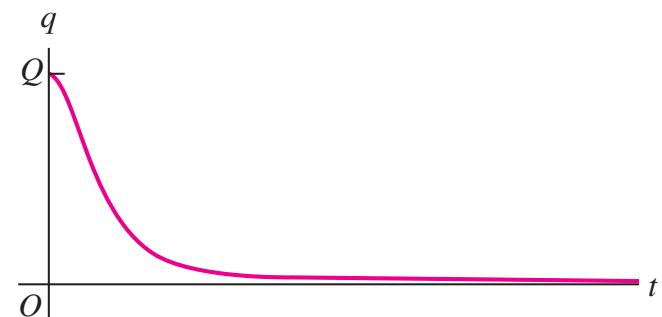(b) Critically damped circuit (larger resistance  $R$ )



$$q = A e^{-(R/2L)t} \cos\left(\sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}t + \phi\right)$$

$$\omega' = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}} \quad (\text{underdamped } L\text{-}R\text{-}C \text{ series circuit})$$