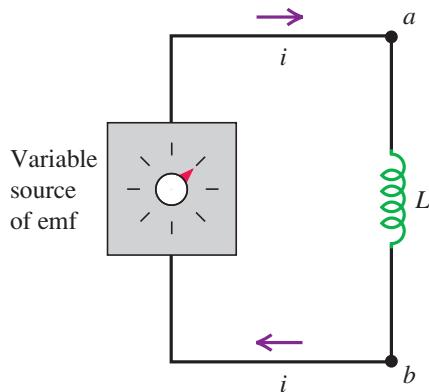



# Chp 30: Inductance - (II)

# Magnetic field energy



an increasing current  $i$  in the inductor causes an emf  $E$  between its terminals and a corresponding potential difference  $V_{ab}$  between the terminals of the source, with point  $a$  at higher potential than point  $b$ . Thus **the source must be adding energy to the inductor**, and the instantaneous power  $P$  (rate of transfer of energy into the inductor) is  $P = V_{ab}i$ .

# Magnetic field energy

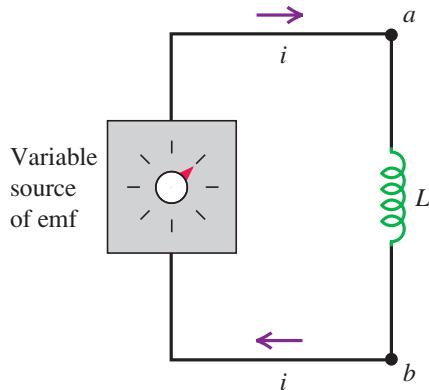


an increasing current  $i$  in the inductor causes an emf  $E$  between its terminals and a corresponding potential difference  $V_{ab}$  between the terminals of the source, with point  $a$  at higher potential than point  $b$ . Thus **the source must be adding energy to the inductor**, and the instantaneous power  $P$  (rate of transfer of energy into the inductor) is  $P = V_{ab}i$ .

We can calculate the total energy input  $U$  needed to establish a final current  $I$  in an inductor with inductance  $L$  if the initial current is zero. We assume that the inductor has zero resistance, so no energy is dissipated within the inductor.

$$di/dt > 0 \quad \rightarrow \quad V_{ab} = L di/dt$$

# Magnetic field energy

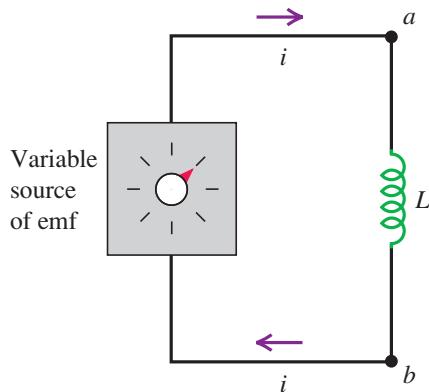

an increasing current  $i$  in the inductor causes an emf  $E$  between its terminals and a corresponding potential difference  $V_{ab}$  between the terminals of the source, with point  $a$  at higher potential than point  $b$ . Thus **the source must be adding energy to the inductor**, and the instantaneous power  $P$  (rate of transfer of energy into the inductor) is  $P = V_{ab}i$ .

We can calculate the total energy input  $U$  needed to establish a final current  $I$  in an inductor with inductance  $L$  if the initial current is zero. We assume that the inductor has zero resistance, so no energy is dissipated within the inductor.


$$di/dt > 0 \quad \rightarrow \quad V_{ab} = L di/dt$$

the rate  $P$  at which energy is being delivered to the inductor (equal to the instantaneous power supplied by the external source) is  $P = V_{ab}i = L i di/dt$

The energy  $dU$  supplied to the inductor during an infinitesimal time interval  $dt$ :  $dU = Pdt$

$$\rightarrow dU = Li di$$

# Magnetic field energy

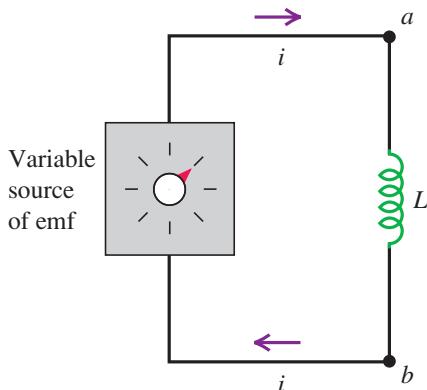

an increasing current  $i$  in the inductor causes an emf  $E$  between its terminals and a corresponding potential difference  $V_{ab}$  between the terminals of the source, with point  $a$  at higher potential than point  $b$ . Thus **the source must be adding energy to the inductor**, and the instantaneous power  $P$  (rate of transfer of energy into the inductor) is  $P = V_{ab}i$ .

We can calculate the total energy input  $U$  needed to establish a final current  $I$  in an inductor with inductance  $L$  if the initial current is zero. We assume that the inductor has zero resistance, so no energy is dissipated within the inductor.

$$di/dt > 0 \rightarrow V_{ab} = L di/dt$$


the rate  $P$  at which energy is being delivered to the inductor (equal to the instantaneous power supplied by the external source) is  $P = V_{ab}i = L i di/dt$

The energy  $dU$  supplied to the inductor during an infinitesimal time interval  $dt$ :  $dU = Pdt$


$$\rightarrow dU = Li di$$

$$\rightarrow U = L \int_0^I i di = \frac{1}{2}LI^2 \quad (\text{energy stored in an inductor})$$

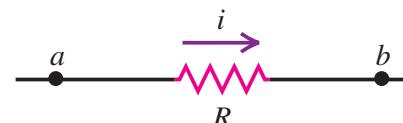Resistor with current  $i$ : energy is *dissipated*.



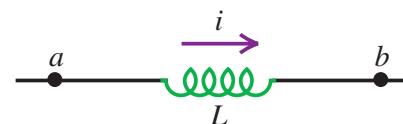Inductor with current  $i$ : energy is *stored*.



# Magnetic Energy Density

The energy in an inductor is actually stored in the magnetic field within the coil, just as the energy of a capacitor is stored in the electric field between its plates. We can develop relationships for magnetic-field energy analogous to those we obtained for electric-field energy

# Magnetic Energy Density

The energy in an inductor is actually stored in the magnetic field within the coil, just as the energy of a capacitor is stored in the electric field between its plates. We can develop relationships for magnetic-field energy analogous to those we obtained for electric-field energy

The volume  $V$  enclosed by the toroidal solenoid is approximately equal to the circumference  $2\pi r$  multiplied by the area  $A$

$$V = 2\pi rA$$

# Magnetic Energy Density

The energy in an inductor is actually stored in the magnetic field within the coil, just as the energy of a capacitor is stored in the electric field between its plates. We can develop relationships for magnetic-field energy analogous to those we obtained for electric-field energy

The volume  $V$  enclosed by the toroidal solenoid is approximately equal to the circumference  $2\pi r$  multiplied by the area  $A$

$$V = 2\pi rA$$

$$L = \frac{\mu_0 N^2 A}{2\pi r} \quad \rightarrow \quad U = \frac{1}{2} L I^2 = \frac{1}{2} \frac{\mu_0 N^2 A}{2\pi r} I^2$$

# Magnetic Energy Density

The energy in an inductor is actually stored in the magnetic field within the coil, just as the energy of a capacitor is stored in the electric field between its plates. We can develop relationships for magnetic-field energy analogous to those we obtained for electric-field energy

The volume  $V$  enclosed by the toroidal solenoid is approximately equal to the circumference  $2\pi r$  multiplied by the area  $A$

$$V = 2\pi rA$$

$$L = \frac{\mu_0 N^2 A}{2\pi r} \rightarrow U = \frac{1}{2} L I^2 = \frac{1}{2} \frac{\mu_0 N^2 A}{2\pi r} I^2$$

The energy per unit volume, is  $u = U/V \rightarrow u = \frac{U}{2\pi r A} = \frac{1}{2} \mu_0 \frac{N^2 I^2}{(2\pi r)^2}$

magnetic energy density,

# Magnetic Energy Density

The energy in an inductor is actually stored in the magnetic field within the coil, just as the energy of a capacitor is stored in the electric field between its plates. We can develop relationships for magnetic-field energy analogous to those we obtained for electric-field energy

The volume  $V$  enclosed by the toroidal solenoid is approximately equal to the circumference  $2\pi r$  multiplied by the area  $A$

$$V = 2\pi rA$$

$$L = \frac{\mu_0 N^2 A}{2\pi r} \rightarrow U = \frac{1}{2} L I^2 = \frac{1}{2} \frac{\mu_0 N^2 A}{2\pi r} I^2$$

The energy per unit volume, is  $u = U/V \rightarrow u = \frac{U}{2\pi r A} = \frac{1}{2} \mu_0 \frac{N^2 I^2}{(2\pi r)^2}$

magnetic energy density,

$$B = \frac{\mu_0 N I}{2\pi r} \rightarrow \frac{N^2 I^2}{(2\pi r)^2} = \frac{B^2}{\mu_0}$$

# Magnetic Energy Density

The energy in an inductor is actually stored in the magnetic field within the coil, just as the energy of a capacitor is stored in the electric field between its plates. We can develop relationships for magnetic-field energy analogous to those we obtained for electric-field energy

The volume  $V$  enclosed by the toroidal solenoid is approximately equal to the circumference  $2\pi r$  multiplied by the area  $A$

$$V = 2\pi rA$$


$$L = \frac{\mu_0 N^2 A}{2\pi r} \rightarrow U = \frac{1}{2} L I^2 = \frac{1}{2} \frac{\mu_0 N^2 A}{2\pi r} I^2$$

The energy per unit volume, is  $u = U/V \rightarrow u = \frac{U}{2\pi r A} = \frac{1}{2} \mu_0 \frac{N^2 I^2}{(2\pi r)^2}$

magnetic energy density,

$$B = \frac{\mu_0 N I}{2\pi r} \rightarrow \frac{N^2 I^2}{(2\pi r)^2} = \frac{B^2}{\mu_0^2}$$
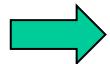
$$u = \frac{B^2}{2\mu_0} \quad (\text{magnetic energy density in vacuum})$$



# Magnetic Energy Density

The energy in an inductor is actually stored in the magnetic field within the coil, just as the energy of a capacitor is stored in the electric field between its plates. We can develop relationships for magnetic-field energy analogous to those we obtained for electric-field energy

The volume  $V$  enclosed by the toroidal solenoid is approximately equal to the circumference  $2\pi r$  multiplied by the area  $A$

$$V = 2\pi rA$$

$$L = \frac{\mu_0 N^2 A}{2\pi r} \rightarrow U = \frac{1}{2} L I^2 = \frac{1}{2} \frac{\mu_0 N^2 A}{2\pi r} I^2$$

The energy per unit volume, is  $u = U/V \rightarrow u = \frac{U}{2\pi r A} = \frac{1}{2} \mu_0 \frac{N^2 I^2}{(2\pi r)^2}$

magnetic energy density,

$$B = \frac{\mu_0 N I}{2\pi r} \rightarrow \frac{N^2 I^2}{(2\pi r)^2} = \frac{B^2}{\mu_0^2}$$

electric energy density:

$$u = \frac{B^2}{2\mu_0} \quad (\text{magnetic energy density in vacuum})$$

$$u = \frac{1}{2} \epsilon_0 E^2$$

# Magnetic Energy Density

The energy in an inductor is actually stored in the magnetic field within the coil, just as the energy of a capacitor is stored in the electric field between its plates. We can develop relationships for magnetic-field energy analogous to those we obtained for electric-field energy

The volume  $V$  enclosed by the toroidal solenoid is approximately equal to the circumference  $2\pi r$  multiplied by the area  $A$

$$V = 2\pi rA$$

$$L = \frac{\mu_0 N^2 A}{2\pi r} \rightarrow U = \frac{1}{2} L I^2 = \frac{1}{2} \frac{\mu_0 N^2 A}{2\pi r} I^2$$

The energy per unit volume, is  $u = U/V \rightarrow u = \frac{U}{2\pi r A} = \frac{1}{2} \mu_0 \frac{N^2 I^2}{(2\pi r)^2}$

magnetic energy density,


$$B = \frac{\mu_0 N I}{2\pi r} \rightarrow \frac{N^2 I^2}{(2\pi r)^2} = \frac{B^2}{\mu_0^2}$$

electric energy density:

$$u = \frac{B^2}{2\mu_0} \quad (\text{magnetic energy density in vacuum})$$

$$u = \frac{1}{2} \epsilon_0 E^2$$
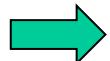
$$u = \frac{B^2}{2\mu} \quad (\text{magnetic energy density in a material})$$



# Magnetic Energy Density

The energy in an inductor is actually stored in the magnetic field within the coil, just as the energy of a capacitor is stored in the electric field between its plates. We can develop relationships for magnetic-field energy analogous to those we obtained for electric-field energy

The volume  $V$  enclosed by the toroidal solenoid is approximately equal to the circumference  $2\pi r$  multiplied by the area  $A$

$$V = 2\pi rA$$

$$L = \frac{\mu_0 N^2 A}{2\pi r} \rightarrow U = \frac{1}{2} L I^2 = \frac{1}{2} \frac{\mu_0 N^2 A}{2\pi r} I^2$$

The energy per unit volume, is  $u = U/V \rightarrow u = \frac{U}{2\pi r A} = \frac{1}{2} \mu_0 \frac{N^2 I^2}{(2\pi r)^2}$

magnetic energy density,

$$B = \frac{\mu_0 N I}{2\pi r} \rightarrow \frac{N^2 I^2}{(2\pi r)^2} = \frac{B^2}{\mu_0^2}$$

electric energy density:

$$u = \frac{B^2}{2\mu_0} \quad (\text{magnetic energy density in vacuum})$$

$$u = \frac{1}{2} \epsilon_0 E^2$$


$$u = \frac{B^2}{2\mu} \quad (\text{magnetic energy density in a material})$$



A primary coil of about 250 turns is connected to the car's battery and produces a strong magnetic field. This coil is surrounded by a secondary coil (25,000 turns). When it is time for a spark plug to fire, an emf of tens of thousands of volts is induced in the secondary coil.
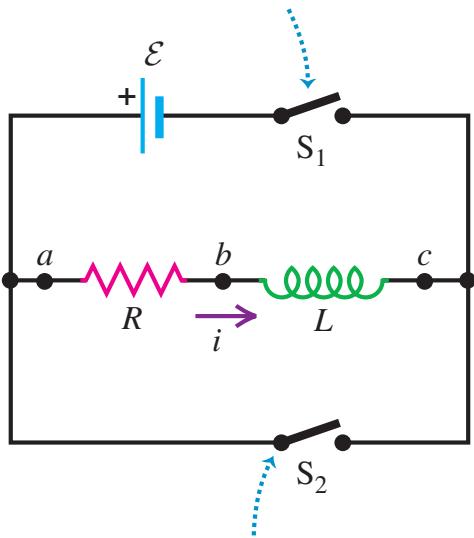
# The $R$ - $L$ circuit

Closing switch  $S_1$  connects the  $R$ - $L$  combination in series with a source of emf  $\mathcal{E}$ .




Closing switch  $S_2$  while opening switch  $S_1$  disconnects the combination from the source.

Suppose both switches are open to begin with, and then at some initial time  $t = 0$  we close switch  $S_1$ . The current cannot change suddenly from zero to some final value, since  $di/dt$  and the induced emf in the inductor would both be infinite. Instead, the current begins to grow at a rate that depends only on the value of  $L$  in the circuit.
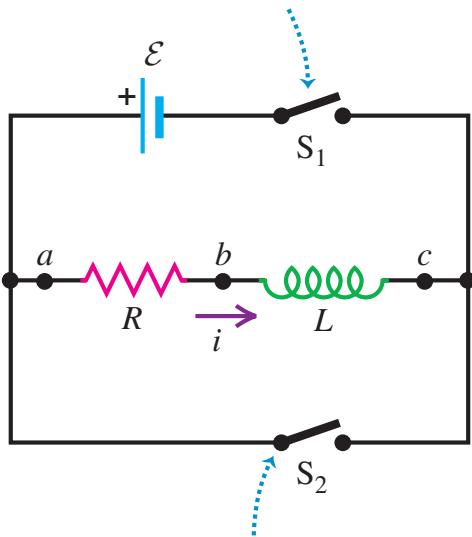
# The $R$ - $L$ circuit

Closing switch  $S_1$  connects the  $R$ - $L$  combination in series with a source of emf  $\mathcal{E}$ .



Closing switch  $S_2$  while opening switch  $S_1$  disconnects the combination from the source.


Suppose both switches are open to begin with, and then at some initial time  $t = 0$  we close switch  $S_1$ . The current cannot change suddenly from zero to some final value, since  $di/dt$  and the induced emf in the inductor would both be infinite. Instead, the current begins to grow at a rate that depends only on the value of  $L$  in the circuit.

The potential difference across the resistor and inductor at that time is

$$v_{ab} = iR \quad v_{bc} = L \frac{di}{dt}$$
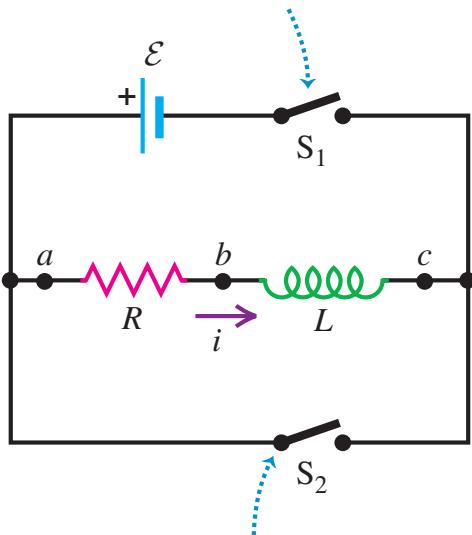
# The $R$ - $L$ circuit

Closing switch  $S_1$  connects the  $R$ - $L$  combination in series with a source of emf  $\mathcal{E}$ .



Closing switch  $S_2$  while opening switch  $S_1$  disconnects the combination from the source.

$$\mathcal{E} - iR - L\frac{di}{dt} = 0$$


Suppose both switches are open to begin with, and then at some initial time  $t = 0$  we close switch  $S_1$ . The current cannot change suddenly from zero to some final value, since  $di/dt$  and the induced emf in the inductor would both be infinite. Instead, the current begins to grow at a rate that depends only on the value of  $L$  in the circuit.

The potential difference across the resistor and inductor at that time is

$$v_{ab} = iR \quad v_{bc} = L\frac{di}{dt}$$
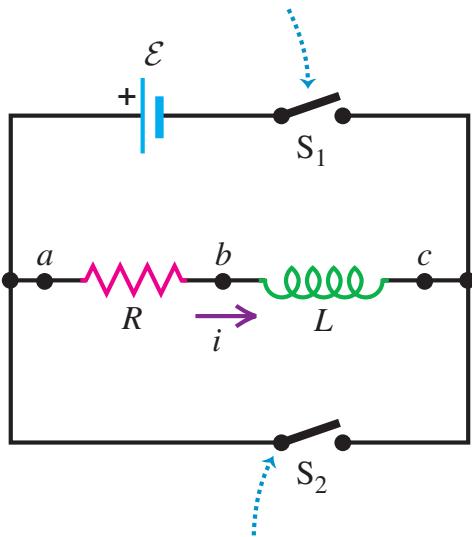
# The $R$ - $L$ circuit

Closing switch  $S_1$  connects the  $R$ - $L$  combination in series with a source of emf  $\mathcal{E}$ .



Closing switch  $S_2$  while opening switch  $S_1$  disconnects the combination from the source.

$$\mathcal{E} - iR - L\frac{di}{dt} = 0 \quad \Rightarrow$$

At the instant that switch  $S_1$  is first closed,  $i=0$   $\Rightarrow$  and the potential drop across  $R$  is zero

Suppose both switches are open to begin with, and then at some initial time  $t=0$  we close switch  $S_1$ . The current cannot change suddenly from zero to some final value, since  $di/dt$  and the induced emf in the inductor would both be infinite. Instead, the current begins to grow at a rate that depends only on the value of  $L$  in the circuit.


The potential difference across the resistor and inductor at that time is

$$v_{ab} = iR \qquad v_{bc} = L\frac{di}{dt}$$

$$\left(\frac{di}{dt}\right)_{\text{initial}} = \frac{\mathcal{E}}{L}$$
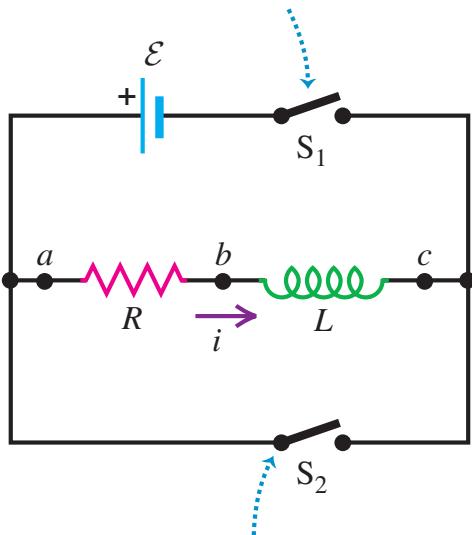
# The $R$ - $L$ circuit

Closing switch  $S_1$  connects the  $R$ - $L$  combination in series with a source of emf  $\mathcal{E}$ .



Closing switch  $S_2$  while opening switch  $S_1$  disconnects the combination from the source.

$$\mathcal{E} - iR - L \frac{di}{dt} = 0 \quad \Rightarrow$$

At the instant that switch  $S_1$  is first closed,  $i=0$   $\Rightarrow$  and the potential drop across  $R$  is zero

$$\left( \frac{di}{dt} \right)_{\text{initial}} = \frac{\mathcal{E}}{L}$$

$$\frac{di}{dt} = \frac{\mathcal{E} - iR}{L} = \frac{\mathcal{E}}{L} - \frac{R}{L}i$$

As the current increases, the term  $(R/L)i$  increases, and the rate of increase of becomes smaller and smaller  $\Rightarrow$  the current is approaching a final, steady-state value  $I$ .


Suppose both switches are open to begin with, and then at some initial time  $t=0$  we close switch  $S_1$ . The current cannot change suddenly from zero to some final value, since  $di/dt$  and the induced emf in the inductor would both be infinite. Instead, the current begins to grow at a rate that depends only on the value of  $L$  in the circuit.

The potential difference across the resistor and inductor at that time is

$$v_{ab} = iR \qquad v_{bc} = L \frac{di}{dt}$$
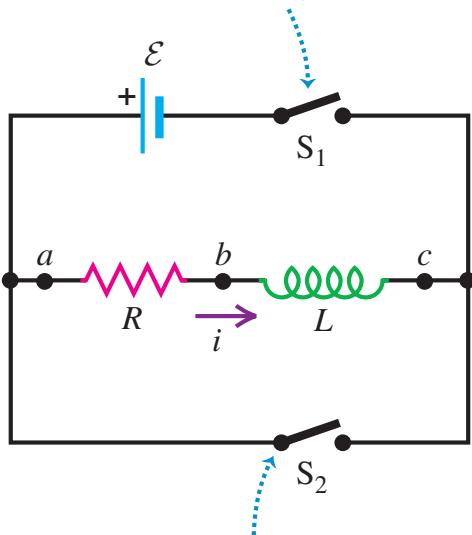
# The $R$ - $L$ circuit

Closing switch  $S_1$  connects the  $R$ - $L$  combination in series with a source of emf  $\mathcal{E}$ .



Closing switch  $S_2$  while opening switch  $S_1$  disconnects the combination from the source.

$$\mathcal{E} - iR - L \frac{di}{dt} = 0 \quad \rightarrow$$

At the instant that switch  $S_1$  is first closed,  $i=0$   $\rightarrow$  and the potential drop across  $R$  is zero

$$\left( \frac{di}{dt} \right)_{\text{initial}} = \frac{\mathcal{E}}{L}$$

$$\frac{di}{dt} = \frac{\mathcal{E} - iR}{L} = \frac{\mathcal{E}}{L} - \frac{R}{L}i$$

As the current increases, the term  $(R/L)i$  increases, and the rate of increase of becomes smaller and smaller  $\rightarrow$  the current is approaching a final, steady-state value  $I$ .

$$\rightarrow \left( \frac{di}{dt} \right)_{\text{final}} = 0 = \frac{\mathcal{E}}{L} - \frac{R}{L}I \quad \leftrightarrow \quad I = \frac{\mathcal{E}}{R}$$


Suppose both switches are open to begin with, and then at some initial time  $t=0$  we close switch  $S_1$ . The current cannot change suddenly from zero to some final value, since  $di/dt$  and the induced emf in the inductor would both be infinite. Instead, the current begins to grow at a rate that depends only on the value of  $L$  in the circuit.

The potential difference across the resistor and inductor at that time is

$$v_{ab} = iR \qquad v_{bc} = L \frac{di}{dt}$$
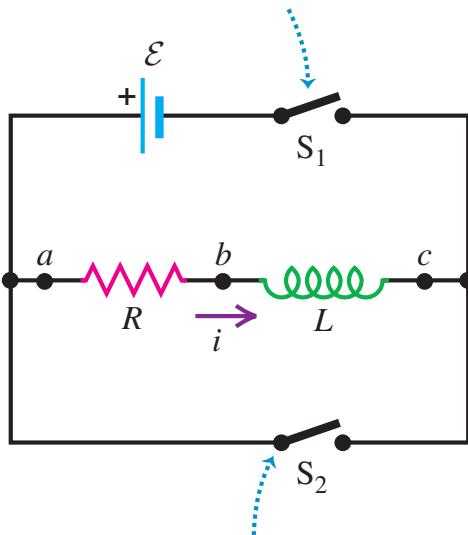
# The $R$ - $L$ circuit

Closing switch  $S_1$  connects the  $R$ - $L$  combination in series with a source of emf  $\mathcal{E}$ .



Closing switch  $S_2$  while opening switch  $S_1$  disconnects the combination from the source.

$$\mathcal{E} - iR - L \frac{di}{dt} = 0 \quad \rightarrow$$

At the instant that switch  $S_1$  is first closed,  $i = 0$   $\rightarrow$  and the potential drop across  $R$  is zero

$$\left( \frac{di}{dt} \right)_{\text{initial}} = \frac{\mathcal{E}}{L}$$

$$\frac{di}{dt} = \frac{\mathcal{E} - iR}{L} = \frac{\mathcal{E}}{L} - \frac{R}{L}i$$



$$\frac{di}{i - (\mathcal{E}/R)} = -\frac{R}{L} dt$$

$$\int_0^i \frac{di'}{i' - (\mathcal{E}/R)} = - \int_0^t \frac{R}{L} dt'$$

Suppose both switches are open to begin with, and then at some initial time  $t = 0$  we close switch  $S_1$ . The current cannot change suddenly from zero to some final value, since  $di/dt$  and the induced emf in the inductor would both be infinite. Instead, the current begins to grow at a rate that depends only on the value of  $L$  in the circuit.

The potential difference across the resistor and inductor at that time is


$$v_{ab} = iR \quad v_{bc} = L \frac{di}{dt}$$

As the current increases, the term  $(R/L)i$  increases, and the rate of increase of becomes smaller and smaller  $\rightarrow$  the current is approaching a final, steady-state value  $I$ .

$$\Rightarrow \left( \frac{di}{dt} \right)_{\text{final}} = 0 = \frac{\mathcal{E}}{L} - \frac{R}{L}I \quad \leftrightarrow \quad I = \frac{\mathcal{E}}{R}$$
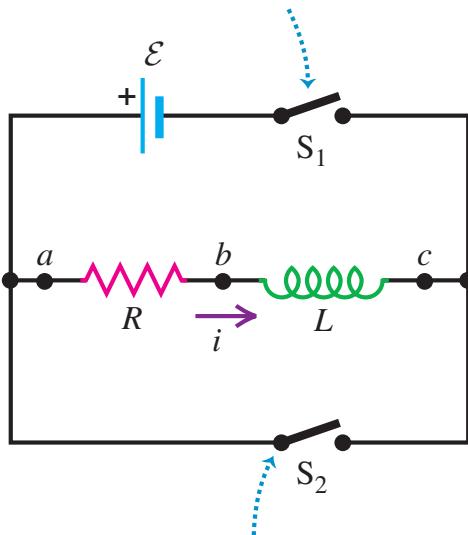
# The $R$ - $L$ circuit

Closing switch  $S_1$  connects the  $R$ - $L$  combination in series with a source of emf  $\mathcal{E}$ .



Closing switch  $S_2$  while opening switch  $S_1$  disconnects the combination from the source.

$$\mathcal{E} - iR - L \frac{di}{dt} = 0 \quad \rightarrow$$

At the instant that switch  $S_1$  is first closed,  $i = 0$   $\rightarrow$  and the potential drop across  $R$  is zero

$$\left( \frac{di}{dt} \right)_{\text{initial}} = \frac{\mathcal{E}}{L}$$

$$\frac{di}{dt} = \frac{\mathcal{E} - iR}{L} = \frac{\mathcal{E}}{L} - \frac{R}{L}i$$



As the current increases, the term  $(R/L)i$  increases, and the rate of increase of becomes smaller and smaller  $\rightarrow$  the current is approaching a final, steady-state value  $I$ .

$$\rightarrow \left( \frac{di}{dt} \right)_{\text{final}} = 0 = \frac{\mathcal{E}}{L} - \frac{R}{L}I \quad \leftrightarrow \quad I = \frac{\mathcal{E}}{R}$$

$$\int_0^i \frac{di'}{i' - (\mathcal{E}/R)} = - \int_0^t \frac{R}{L} dt' \quad \rightarrow \quad \ln \left( \frac{i - (\mathcal{E}/R)}{-\mathcal{E}/R} \right) = - \frac{R}{L} t$$


Suppose both switches are open to begin with, and then at some initial time  $t = 0$  we close switch  $S_1$ . The current cannot change suddenly from zero to some final value, since  $di/dt$  and the induced emf in the inductor would both be infinite. Instead, the current begins to grow at a rate that depends only on the value of  $L$  in the circuit.

The potential difference across the resistor and inductor at that time is

$$v_{ab} = iR \quad v_{bc} = L \frac{di}{dt}$$
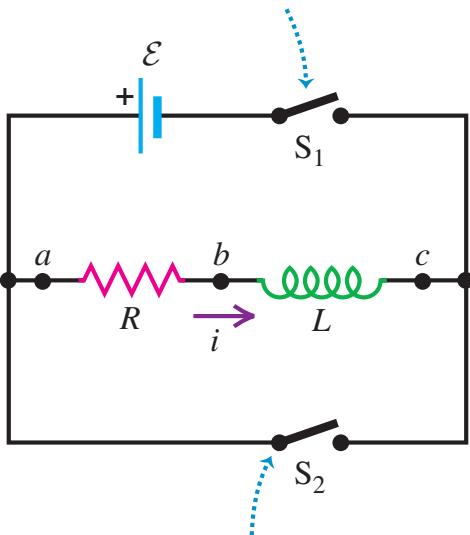
# The $R$ - $L$ circuit

Closing switch  $S_1$  connects the  $R$ - $L$  combination in series with a source of emf  $\mathcal{E}$ .



Closing switch  $S_2$  while opening switch  $S_1$  disconnects the combination from the source.

$$\mathcal{E} - iR - L \frac{di}{dt} = 0 \quad \rightarrow$$

At the instant that switch  $S_1$  is first closed,  $i=0$   $\rightarrow$  and the potential drop across  $R$  is zero

$$\left( \frac{di}{dt} \right)_{\text{initial}} = \frac{\mathcal{E}}{L}$$

$$\frac{di}{dt} = \frac{\mathcal{E} - iR}{L} = \frac{\mathcal{E}}{L} - \frac{R}{L}i$$



$$\frac{di}{i - (\mathcal{E}/R)} = -\frac{R}{L} dt$$

$$\int_0^i \frac{di'}{i' - (\mathcal{E}/R)} = - \int_0^t \frac{R}{L} dt' \quad \rightarrow \quad \ln \left( \frac{i - (\mathcal{E}/R)}{-\mathcal{E}/R} \right) = -\frac{R}{L} t \quad \rightarrow \quad i = \frac{\mathcal{E}}{R} \left( 1 - e^{-(R/L)t} \right)$$

Suppose both switches are open to begin with, and then at some initial time  $t=0$  we close switch  $S_1$ . The current cannot change suddenly from zero to some final value, since  $di/dt$  and the induced emf in the inductor would both be infinite. Instead, the current begins to grow at a rate that depends only on the value of  $L$  in the circuit.


The potential difference across the resistor and inductor at that time is

$$v_{ab} = iR \quad v_{bc} = L \frac{di}{dt}$$

As the current increases, the term  $(R/L)i$  increases, and the rate of increase of becomes smaller and smaller  $\rightarrow$  the current is approaching a final, steady-state value  $I$ .


$$\rightarrow \left( \frac{di}{dt} \right)_{\text{final}} = 0 = \frac{\mathcal{E}}{L} - \frac{R}{L}I \quad \leftrightarrow \quad I = \frac{\mathcal{E}}{R}$$

Switch  $S_1$  is closed at  $t = 0$ .

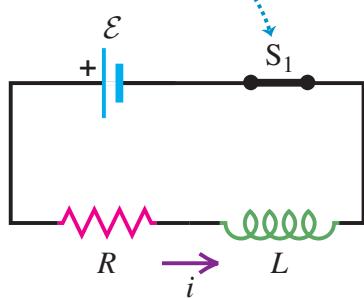


$$i = \frac{\mathcal{E}}{R} (1 - e^{-(R/L)t})$$

current in an  $R-L$  circuit with emf

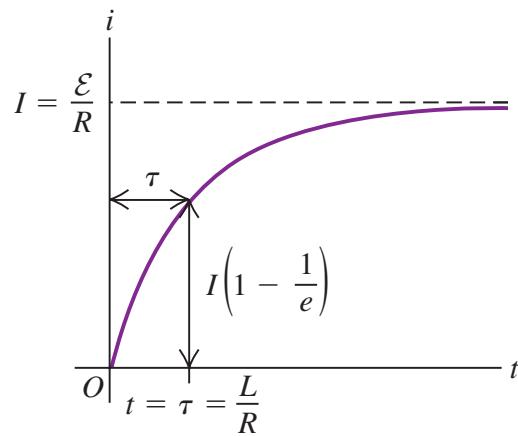

Switch  $S_1$  is closed at  $t = 0$ .

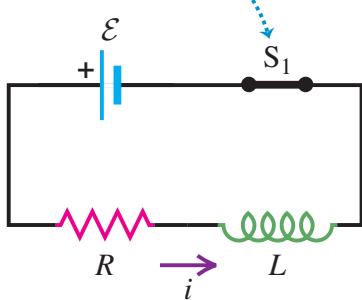


$$i = \frac{\mathcal{E}}{R} (1 - e^{-(R/L)t})$$


current in an  $R-L$  circuit with emf

$$\rightarrow \frac{di}{dt} = \frac{\mathcal{E}}{L} e^{-(R/L)t}$$

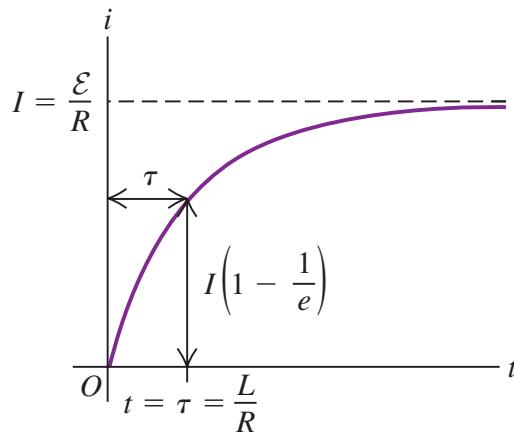At time  $t = 0, I = 0$  and  $di/dt = \mathcal{E}/L$ . As  $t \rightarrow \infty$ ,  $i \rightarrow \mathcal{E}/L$  and  $idt \rightarrow 0$ ,




Switch  $S_1$  is closed at  $t = 0$ .

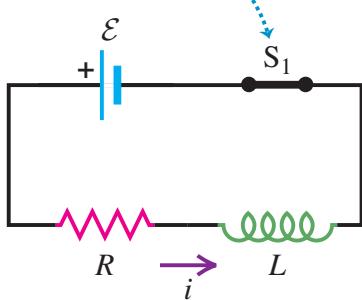

$$i = \frac{\mathcal{E}}{R} (1 - e^{-(R/L)t})$$

current in an  $R-L$  circuit with emf
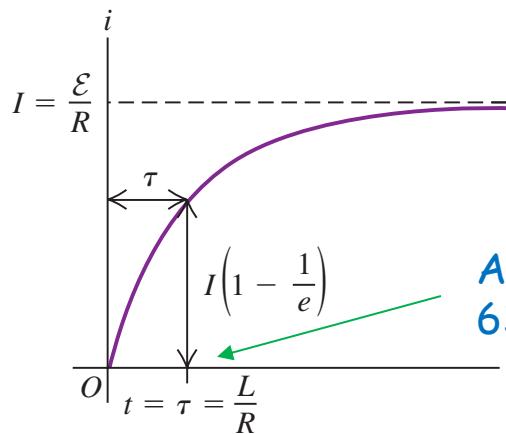
$$\rightarrow \frac{di}{dt} = \frac{\mathcal{E}}{L} e^{-(R/L)t}$$




At time  $t = 0, I = 0$  and  $di/dt = \mathcal{E}/L$ . As  $t \rightarrow \infty, i \rightarrow \mathcal{E}/L$  and  $idt \rightarrow 0$ ,

$$\tau = \frac{L}{R} \quad (\text{time constant for an } R-L \text{ circuit})$$

At a time equal to  $L/R$ , the current has risen to  $(1 - 1/e)$ , or about 63%, of its final value


Switch  $S_1$  is closed at  $t = 0$ .

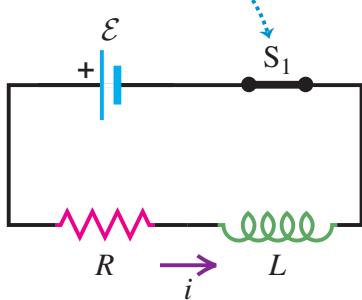

$$i = \frac{\mathcal{E}}{R} (1 - e^{-(R/L)t})$$

current in an  $R-L$  circuit with emf
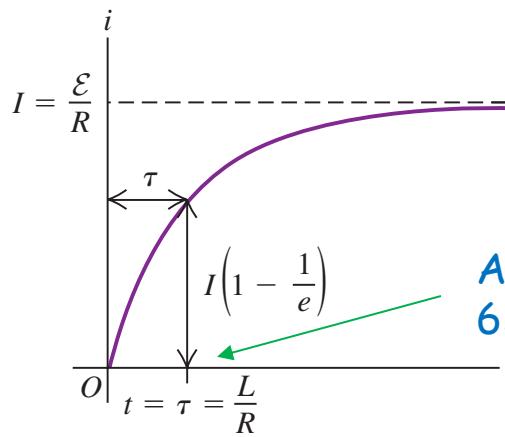
$$\rightarrow \frac{di}{dt} = \frac{\mathcal{E}}{L} e^{-(R/L)t}$$



At time  $t = 0$ ,  $I = 0$  and  $di/dt = \mathcal{E}/L$ . As  $t \rightarrow \infty$ ,  $i \rightarrow \mathcal{E}/L$  and  $idt \rightarrow 0$ ,


$$\tau = \frac{L}{R} \quad (\text{time constant for an } R-L \text{ circuit})$$

At a time equal to  $L/R$ , the current has risen to  $(1 - 1/e)$ , or about 63%, of its final value

For example, if  $R = 100 \Omega$  and  $L = 10 \text{ H}$

$$\tau = \frac{L}{R} = \frac{10 \text{ H}}{100 \Omega} = 0.10 \text{ s}$$


Switch  $S_1$  is closed at  $t = 0$ .

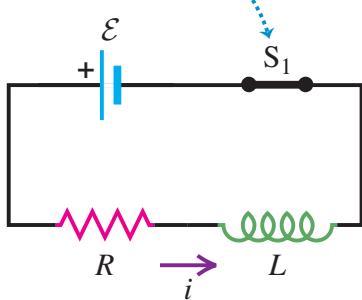

$$i = \frac{\mathcal{E}}{R} (1 - e^{-(R/L)t})$$

current in an  $R-L$  circuit with emf
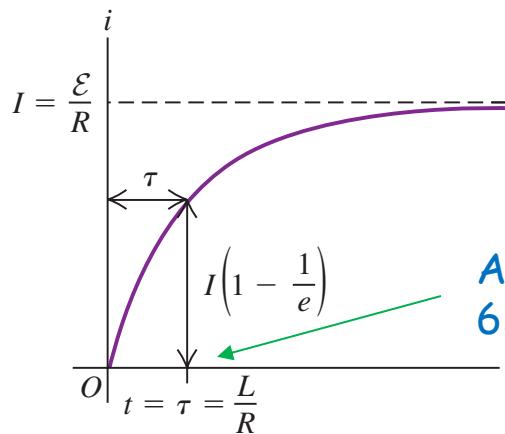
$$\rightarrow \frac{di}{dt} = \frac{\mathcal{E}}{L} e^{-(R/L)t}$$



At time  $t = 0$ ,  $I = 0$  and  $di/dt = \mathcal{E}/L$ . As  $t \rightarrow \infty$ ,  $i \rightarrow \mathcal{E}/L$  and  $idt \rightarrow 0$ ,

$$\tau = \frac{L}{R} \quad (\text{time constant for an } R-L \text{ circuit})$$


At a time equal to  $L/R$ , the current has risen to  $(1 - 1/e)$ , or about 63%, of its final value

For example, if  $R = 100 \Omega$  and  $L = 10 \text{ H}$        $\tau = \frac{L}{R} = \frac{10 \text{ H}}{100 \Omega} = 0.10 \text{ s}$

Meaning the current increases to about 63% of its final value in 0.10 s.

(Recall that  $1 \text{ H} = 1 \Omega \text{ s}$ .) If  $L = 0.010 \text{ H}$ ,  $t = 10^{-4} \text{ s} = 0.10 \text{ ms}$ , and the rise is much more rapid.


Switch  $S_1$  is closed at  $t = 0$ .

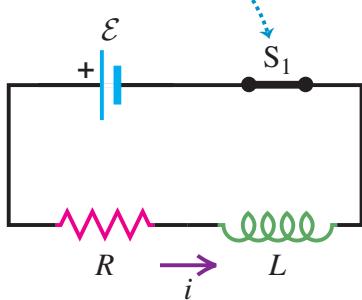

$$i = \frac{\mathcal{E}}{R} (1 - e^{-(R/L)t})$$

current in an  $R-L$  circuit with emf
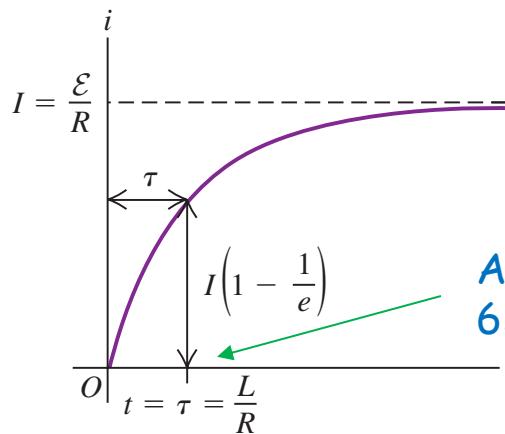
$$\rightarrow \frac{di}{dt} = \frac{\mathcal{E}}{L} e^{-(R/L)t}$$



At time  $t = 0$ ,  $I = 0$  and  $di/dt = \mathcal{E}/L$ . As  $t \rightarrow \infty$ ,  $i \rightarrow \mathcal{E}/L$  and  $idt \rightarrow 0$ ,

$$\tau = \frac{L}{R} \quad (\text{time constant for an } R-L \text{ circuit})$$

At a time equal to  $L/R$ , the current has risen to  $(1 - 1/e)$ , or about 63%, of its final value

For example, if  $R = 100 \Omega$  and  $L = 10 \text{ H}$        $\tau = \frac{L}{R} = \frac{10 \text{ H}}{100 \Omega} = 0.10 \text{ s}$


Meaning the current increases to about 63% of its final value in 0.10 s.

(Recall that  $1 \text{ H} = 1 \Omega \text{ s}$ .) If  $L = 0.010 \text{ H}$ ,  $t = 10^{-4} \text{ s} = 0.10 \text{ ms}$ , and the rise is much more rapid.

The instantaneous rate at which the source delivers energy to the circuit is  $P = \mathcal{E}i$ . The instantaneous rate at which energy is dissipated in the resistor is  $P_R$ , and the rate at which energy is stored in the inductor is  $iV_{bc} = Li di/dt$

$$\mathcal{E} - iR - L \frac{di}{dt} = 0 \quad \rightarrow \quad \mathcal{E}i = i^2R + Li \frac{di}{dt}$$

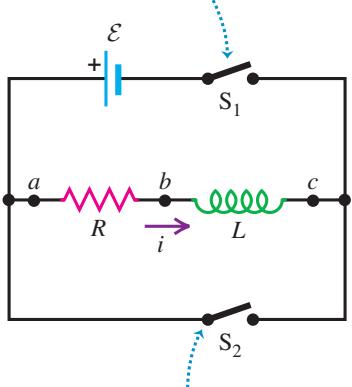Closing switch  $S_1$  connects the  $R-L$  combination in series with a source of emf  $\mathcal{E}$ .



Closing switch  $S_2$  while opening switch  $S_1$  disconnects the combination from the source.


## Analyzing an R-L circuit

A sensitive electronic device of resistance  $R = 175 \Omega$  is to be connected to a source of emf (of negligible internal resistance) by a switch. The device is designed to operate with a  $36\text{-mA}$  current, but to avoid damage to the device, the current can rise to no more than  $4.9\text{ mA}$  in the first  $58\text{ }\mu\text{s}$  after the switch is closed. An inductor is therefore connected in series with the device, as in figure the switch in question is  $S_1$ .

- What is the required source emf  $\mathcal{E}$ ? (b)
- What is the required inductance  $L$ ? (c) What is time constant  $T$ ?
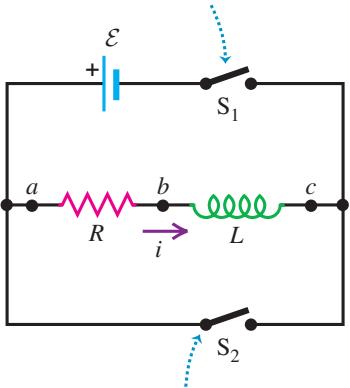
# Analyzing an R-L circuit

Closing switch  $S_1$  connects the  $R$ - $L$  combination in series with a source of emf  $\mathcal{E}$ .




Closing switch  $S_2$  while opening switch  $S_1$  disconnects the combination from the source.

A sensitive electronic device of resistance  $R = 175 \Omega$  is to be connected to a source of emf (of negligible internal resistance) by a switch. The device is designed to operate with a 36-mA current, but to avoid damage to the device, the current can rise to no more than 4.9 mA in the first  $58 \mu\text{s}$  after the switch is closed. An inductor is therefore connected in series with the device, as in figure the switch in question is  $S_1$ .

(a) What is the required source emf  $\mathcal{E}$ ? (b)

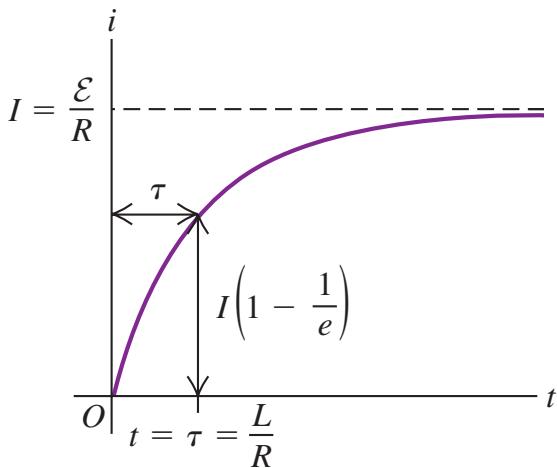(b) What is the required inductance  $L$ ? (c) What is time constant  $T$ ?




(a) Final current  $I = \mathcal{E}/R \rightarrow \mathcal{E} = IR = (0.036 \text{ A})(175 \Omega) = 6.3 \text{ V}$

$$i = \frac{\mathcal{E}}{R} \left(1 - e^{-(R/L)t}\right)$$
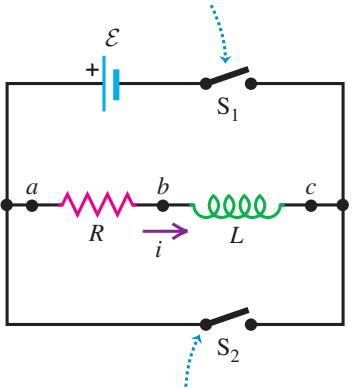
# Analyzing an R-L circuit

Closing switch  $S_1$  connects the  $R$ - $L$  combination in series with a source of emf  $\mathcal{E}$ .




Closing switch  $S_2$  while opening switch  $S_1$  disconnects the combination from the source.

A sensitive electronic device of resistance  $R = 175 \Omega$  is to be connected to a source of emf (of negligible internal resistance) by a switch. The device is designed to operate with a 36-mA current, but to avoid damage to the device, the current can rise to no more than 4.9 mA in the first  $58 \mu\text{s}$  after the switch is closed. An inductor is therefore connected in series with the device, as in figure the switch in question is  $S_1$ .

(a) What is the required source emf  $\mathcal{E}$ ? (b)

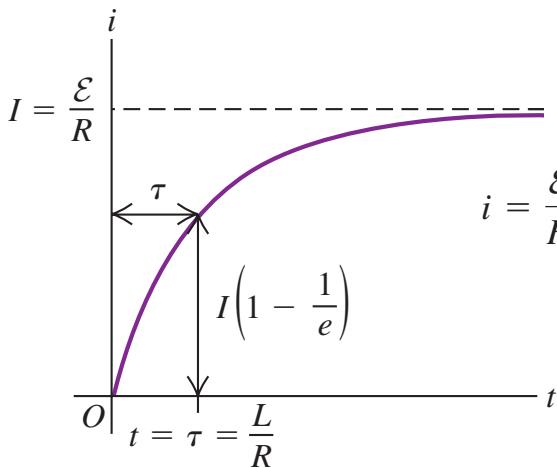
(b) What is the required inductance  $L$ ? (c) What is time constant  $\tau$ ?



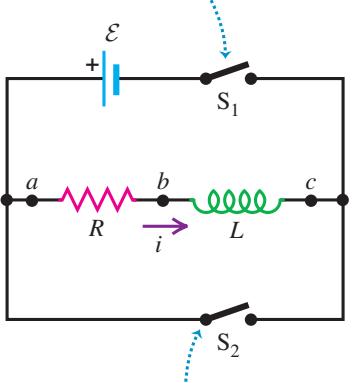(a) Final current  $I = \mathcal{E}/R \rightarrow \mathcal{E} = IR = (0.036 \text{ A})(175 \Omega) = 6.3 \text{ V}$

$$i = \frac{\mathcal{E}}{R}(1 - e^{-(R/L)t}) \quad \Rightarrow \quad 1 - \frac{iR}{\mathcal{E}} = e^{-(R/L)t} \quad \Rightarrow \quad L = \frac{-Rt}{\ln(1 - iR/\mathcal{E})}$$

Closing switch  $S_1$  connects the  $R-L$  combination in series with a source of emf  $\mathcal{E}$ .




Closing switch  $S_2$  while opening switch  $S_1$  disconnects the combination from the source.

## Analyzing an R-L circuit

A sensitive electronic device of resistance  $R = 175 \Omega$  is to be connected to a source of emf (of negligible internal resistance) by a switch. The device is designed to operate with a 36-mA current, but to avoid damage to the device, the current can rise to no more than 4.9 mA in the first  $58 \mu\text{s}$  after the switch is closed. An inductor is therefore connected in series with the device, as in figure the switch in question is  $S_1$ .

(a) What is the required source emf  $\mathcal{E}$ ? (b)

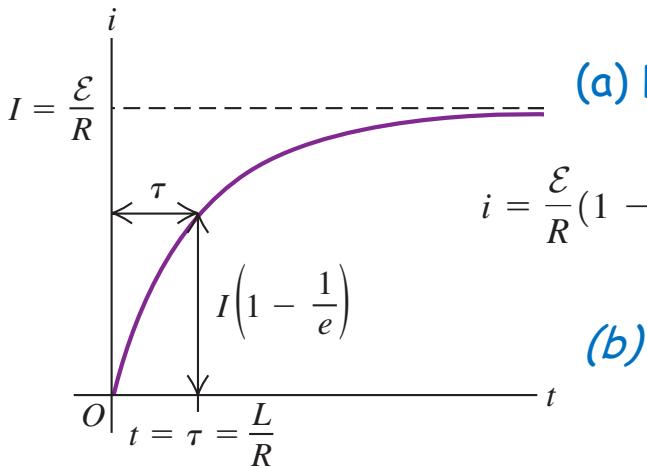(b) What is the required inductance  $L$ ? (c) What is time constant  $\tau$ ?




$$(a) \text{Final current } I = \mathcal{E}/R \rightarrow \mathcal{E} = IR = (0.036 \text{ A})(175 \Omega) = 6.3 \text{ V}$$

$$i = \frac{\mathcal{E}}{R}(1 - e^{-(R/L)t}) \rightarrow 1 - \frac{iR}{\mathcal{E}} = e^{-(R/L)t} \rightarrow L = \frac{-Rt}{\ln(1 - iR/\mathcal{E})}$$

(b)

$$L = \frac{-(175 \Omega)(58 \times 10^{-6} \text{ s})}{\ln[1 - (4.9 \times 10^{-3} \text{ A})(175 \Omega)/(6.3 \text{ V})]} = 69 \text{ mH}$$

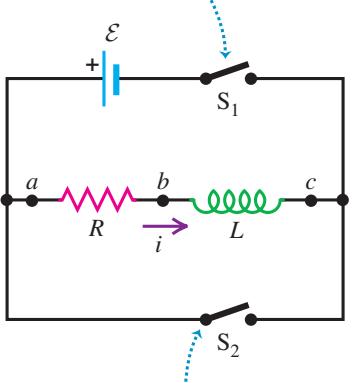Closing switch  $S_1$  connects the  $R-L$  combination in series with a source of emf  $\mathcal{E}$ .




Closing switch  $S_2$  while opening switch  $S_1$  disconnects the combination from the source.

## Analyzing an R-L circuit

A sensitive electronic device of resistance  $R = 175 \Omega$  is to be connected to a source of emf (of negligible internal resistance) by a switch. The device is designed to operate with a 36-mA current, but to avoid damage to the device, the current can rise to no more than 4.9 mA in the first  $58 \mu\text{s}$  after the switch is closed. An inductor is therefore connected in series with the device, as in figure the switch in question is  $S_1$ .

(a) What is the required source emf  $\mathcal{E}$ ? (b)

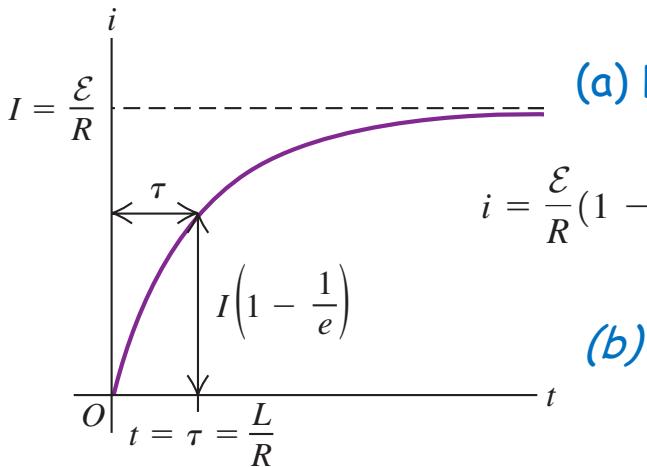(b) What is the required inductance  $L$ ? (c) What is time constant  $\tau$ ?




$$(a) \text{ Final current } I = \mathcal{E}/R \rightarrow \mathcal{E} = IR = (0.036 \text{ A})(175 \Omega) = 6.3 \text{ V}$$

$$i = \frac{\mathcal{E}}{R}(1 - e^{-(R/L)t}) \rightarrow 1 - \frac{iR}{\mathcal{E}} = e^{-(R/L)t} \rightarrow L = \frac{-Rt}{\ln(1 - iR/\mathcal{E})}$$

$$(b) L = \frac{-(175 \Omega)(58 \times 10^{-6} \text{ s})}{\ln[1 - (4.9 \times 10^{-3} \text{ A})(175 \Omega)/(6.3 \text{ V})]} = 69 \text{ mH}$$

$$(c) \tau = \frac{L}{R} = \frac{69 \times 10^{-3} \text{ H}}{175 \Omega} = 3.9 \times 10^{-4} \text{ s} = 390 \mu\text{s}$$

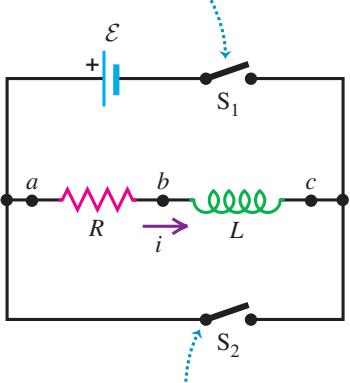Closing switch  $S_1$  connects the  $R-L$  combination in series with a source of emf  $\mathcal{E}$ .




Closing switch  $S_2$  while opening switch  $S_1$  disconnects the combination from the source.

## Analyzing an R-L circuit

A sensitive electronic device of resistance  $R = 175 \Omega$  is to be connected to a source of emf (of negligible internal resistance) by a switch. The device is designed to operate with a 36-mA current, but to avoid damage to the device, the current can rise to no more than 4.9 mA in the first  $58 \mu\text{s}$  after the switch is closed. An inductor is therefore connected in series with the device, as in figure the switch in question is  $S_1$ .

(a) What is the required source emf  $\mathcal{E}$ ? (b)

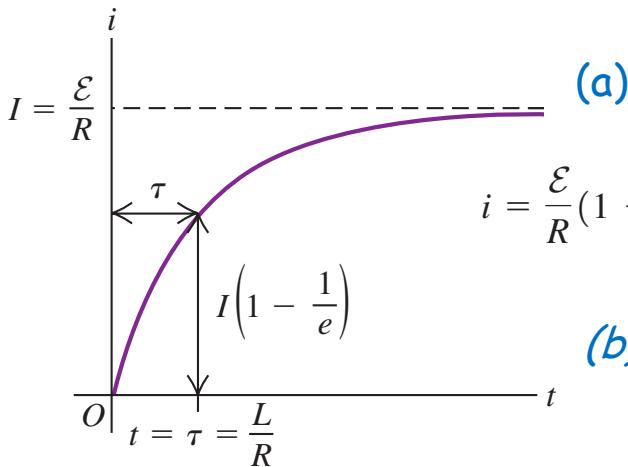(b) What is the required inductance  $L$ ? (c) What is time constant  $\tau$ ?



$$(a) \text{ Final current } I = \mathcal{E}/R \rightarrow \mathcal{E} = IR = (0.036 \text{ A})(175 \Omega) = 6.3 \text{ V}$$

$$i = \frac{\mathcal{E}}{R}(1 - e^{-(R/L)t}) \rightarrow 1 - \frac{iR}{\mathcal{E}} = e^{-(R/L)t} \rightarrow L = \frac{-Rt}{\ln(1 - iR/\mathcal{E})}$$


$$(b) L = \frac{-(175 \Omega)(58 \times 10^{-6} \text{ s})}{\ln[1 - (4.9 \times 10^{-3} \text{ A})(175 \Omega)/(6.3 \text{ V})]} = 69 \text{ mH}$$

$$(c) \tau = \frac{L}{R} = \frac{69 \times 10^{-3} \text{ H}}{175 \Omega} = 3.9 \times 10^{-4} \text{ s} = 390 \mu\text{s}$$

Note that  $58 \mu\text{s}$  is much less than the time constant ( $390 \mu\text{s}$ ). In  $58 \mu\text{s}$  the current builds up from zero to 4.9 mA, a small fraction of its final value of 36 mA; after  $390 \mu\text{s}$  the current equals  $(1 - 1/e)$  of its final value, or about  $(0.63)(36 \text{ mA}) = 23 \text{ mA}$ .

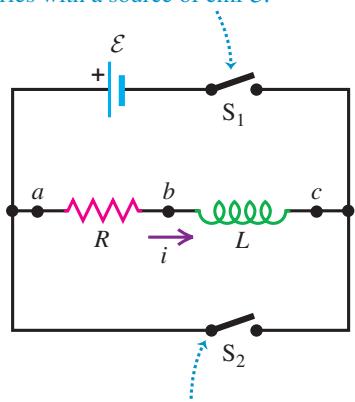
# Current Decay in an R-L Circuit

Closing switch  $S_1$  connects the  $R$ - $L$  combination in series with a source of emf  $\mathcal{E}$ .




Closing switch  $S_2$  while opening switch  $S_1$  disconnects the combination from the source.

Switch  $S_1$  is closed at  $t = 0$ .

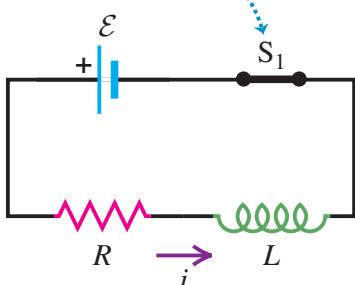


charging

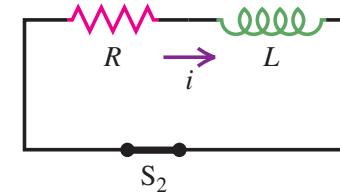

decaying


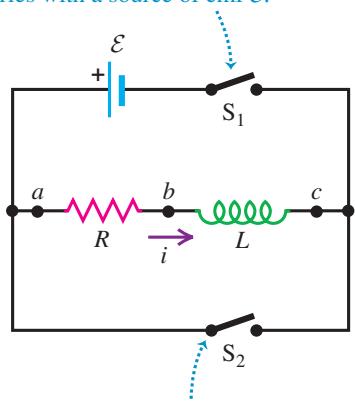
# Current Decay in an R-L Circuit

Closing switch  $S_1$  connects the  $R$ - $L$  combination in series with a source of emf  $\mathcal{E}$ .



Closing switch  $S_2$  while opening switch  $S_1$  disconnects the combination from the source.

Switch  $S_1$  is closed at  $t = 0$ .

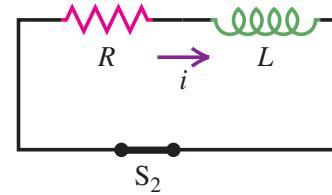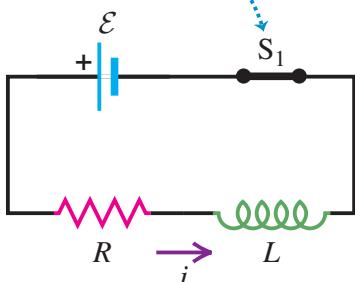


decaying

charging

$$\mathcal{E} - iR - L \frac{di}{dt} = 0$$

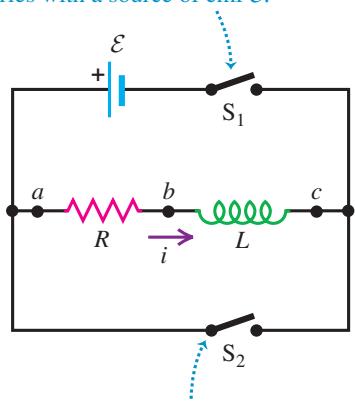
# Current Decay in an R-L Circuit

Closing switch  $S_1$  connects the  $R$ - $L$  combination in series with a source of emf  $\mathcal{E}$ .




Closing switch  $S_2$  while opening switch  $S_1$  disconnects the combination from the source.

Switch  $S_1$  is closed at  $t = 0$ .

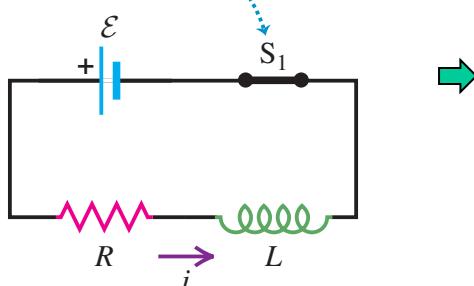

charging
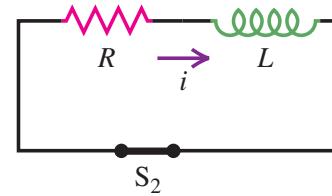
$$\mathcal{E} - iR - L \frac{di}{dt} = 0$$




decaying

$$-iR - L \frac{di}{dt} = 0$$


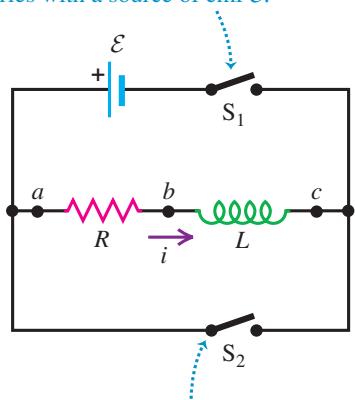
# Current Decay in an R-L Circuit

Closing switch  $S_1$  connects the  $R$ - $L$  combination in series with a source of emf  $\mathcal{E}$ .



Closing switch  $S_2$  while opening switch  $S_1$  disconnects the combination from the source.

Switch  $S_1$  is closed at  $t = 0$ .

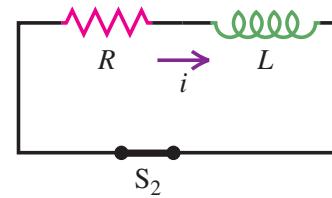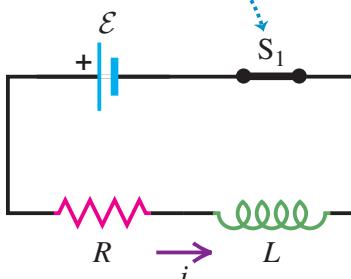

decaying

charging


$$\mathcal{E} - iR - L \frac{di}{dt} = 0$$

$$-iR - L \frac{di}{dt} = 0$$


$$\Rightarrow i = I_0 e^{-(R/L)t}$$
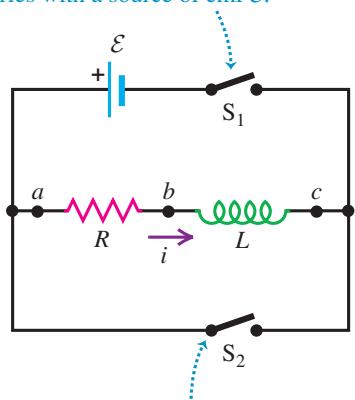
# Current Decay in an R-L Circuit


Closing switch  $S_1$  connects the  $R$ - $L$  combination in series with a source of emf  $\mathcal{E}$ .



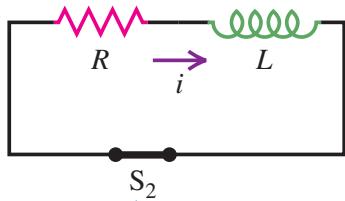Closing switch  $S_2$  while opening switch  $S_1$  disconnects the combination from the source.



Switch  $S_1$  is closed at  $t = 0$ .

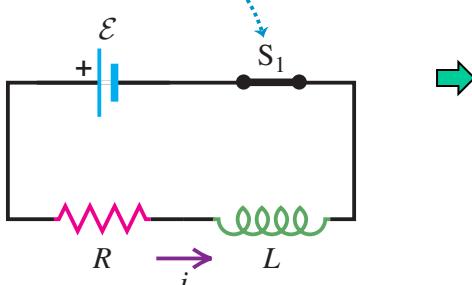

charging


$$\mathcal{E} - iR - L \frac{di}{dt} = 0$$

$$-iR - L \frac{di}{dt} = 0$$

decaying


$$\Rightarrow i = I_0 e^{-(R/L)t}$$

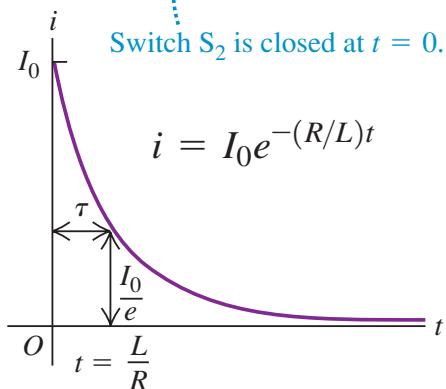$I_0$  is the initial current at time  $t = 0$



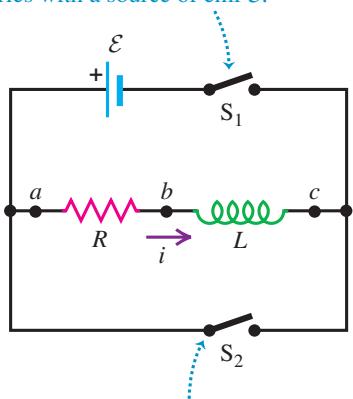
# Current Decay in an R-L Circuit



Closing switch  $S_1$  connects the  $R$ - $L$  combination in series with a source of emf  $\mathcal{E}$ .



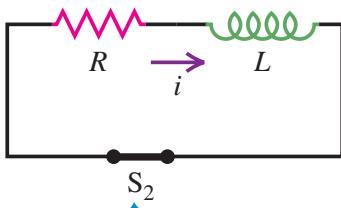Closing switch  $S_2$  while opening switch  $S_1$  disconnects the combination from the source.



Switch  $S_1$  is closed at  $t = 0$ .

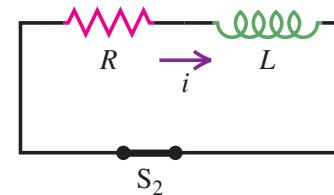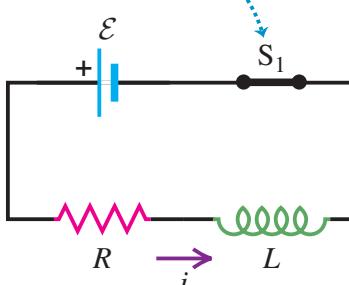

decaying

charging


$$\mathcal{E} - iR - L \frac{di}{dt} = 0$$

$$-iR - L \frac{di}{dt} = 0$$

$$\Rightarrow i = I_0 e^{-(R/L)t}$$

$I_0$  is the initial current at time  $t = 0$

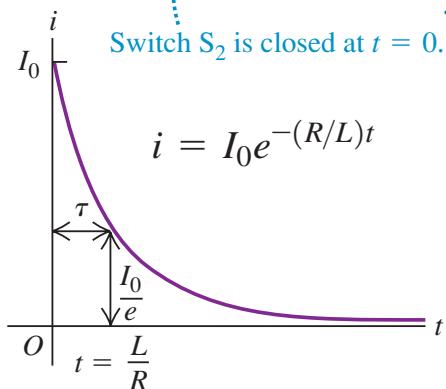
The time constant,  $\tau = L/R$  is the time for current to decrease to  $1/e$  or about 37%, of its original value




$$i = I_0 e^{-(R/L)t}$$
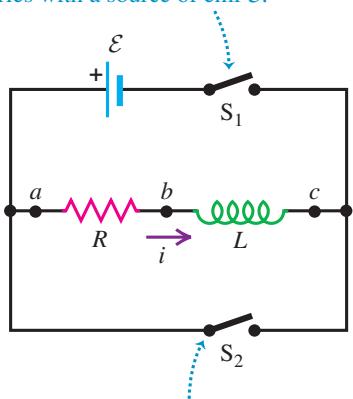
# Current Decay in an R-L Circuit



Closing switch  $S_1$  connects the  $R$ - $L$  combination in series with a source of emf  $\mathcal{E}$ .



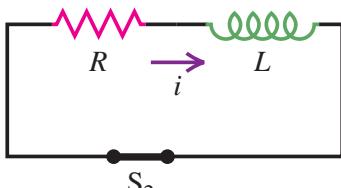Closing switch  $S_2$  while opening switch  $S_1$  disconnects the combination from the source.



Switch  $S_1$  is closed at  $t = 0$ .

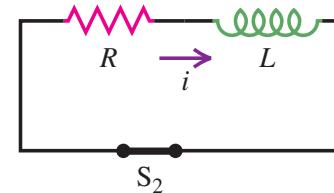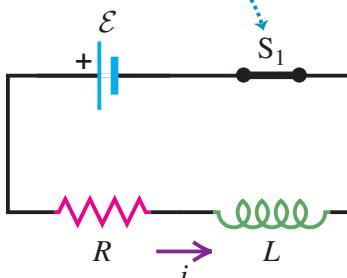

decaying

charging


$$\mathcal{E} - iR - L \frac{di}{dt} = 0$$

$$-iR - L \frac{di}{dt} = 0$$

$$\Rightarrow i = I_0 e^{-(R/L)t}$$

$I_0$  is the initial current at time  $t = 0$

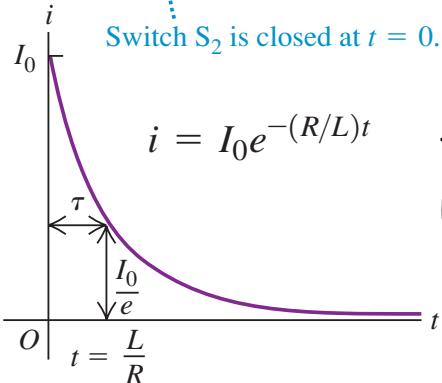The time constant,  $\tau = L/R$  is the time for current to decrease to  $1/e$  or about 37%, of its original value




The energy that is needed to maintain the current during this decay is provided by the energy stored in the magnetic field of the inductor


$$0 = i^2 R + L i \frac{di}{dt}$$
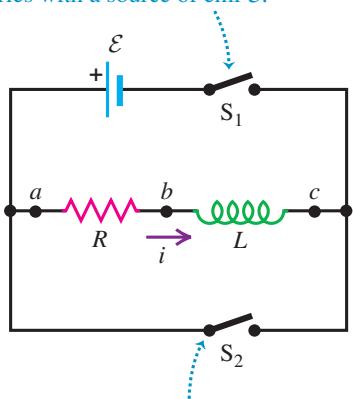
# Current Decay in an R-L Circuit



Closing switch  $S_1$  connects the  $R-L$  combination in series with a source of emf  $\mathcal{E}$ .



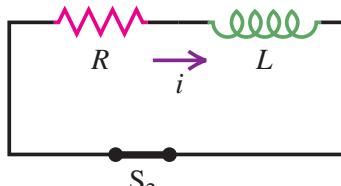Closing switch  $S_2$  while opening switch  $S_1$  disconnects the combination from the source.



Switch  $S_1$  is closed at  $t = 0$ .

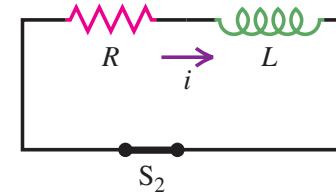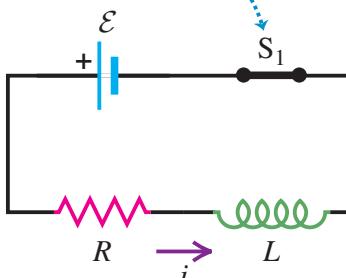

decaying


$$\mathcal{E} - iR - L \frac{di}{dt} = 0$$

$$-iR - L \frac{di}{dt} = 0$$

➡  $i = I_0 e^{-(R/L)t}$

$I_0$  is the initial current at time  $t = 0$

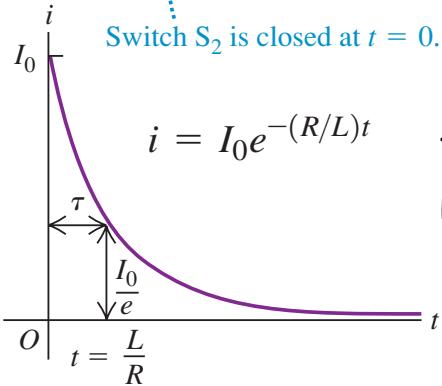The time constant,  $\tau = L/R$  is the time for current to decrease to  $1/e$  or about 37%, of its original value



The energy that is needed to maintain the current during this decay is provided by the energy stored in the magnetic field of the inductor

$$0 = i^2 R + L i \frac{di}{dt}$$

the energy stored in the inductor **decreases** at a rate equal to the rate of dissipation of energy  $i^2 R$  in the resistor.