

Chp 24: Capacitance and Dielectrics

Goals for Chapter 24


- To understand capacitors and calculate capacitance
- To analyze networks of capacitors
- To calculate the energy stored in a capacitor
- To examine dielectrics and how they affect capacitance

Capacitors and Capacitance



Capacitors are devices that **store electric potential energy**.
The energy of a capacitor is actually stored in the electric field.

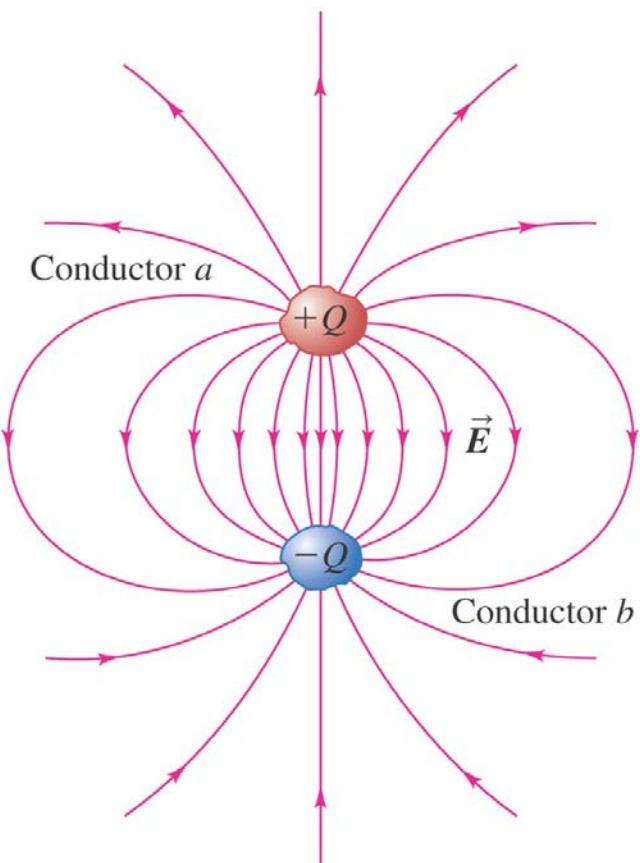In circuit diagrams a capacitor is represented by either of
these symbols:




Capacitors and Capacitance



Capacitors are devices that **store electric potential energy**.
The energy of a capacitor is actually stored in the electric field.

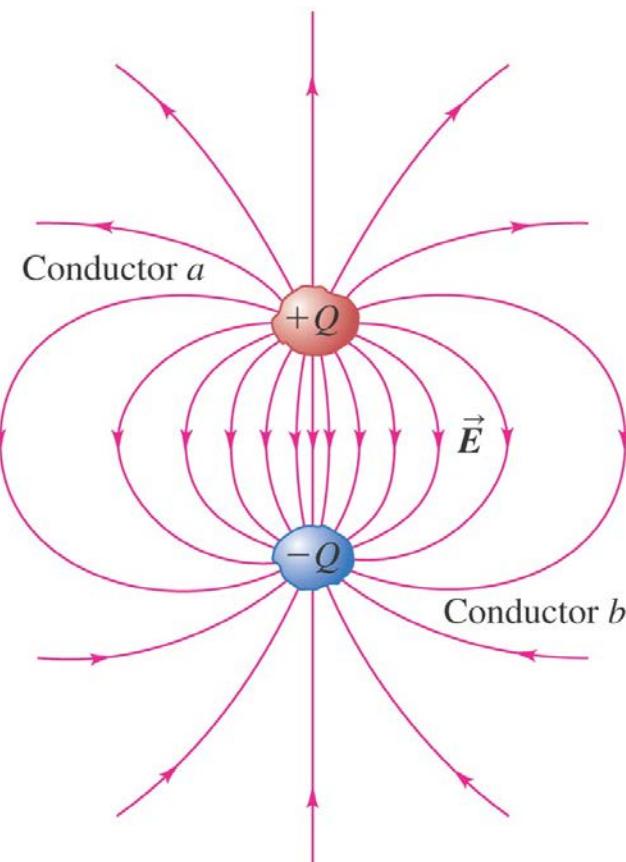In circuit diagrams a capacitor is represented by either of these symbols:




- Any two conductors separated by an insulator form a *capacitor*
- The definition of capacitance is $C = Q/V_{ab}$

$$C = \frac{Q}{V_{ab}} \quad (\text{definition of capacitance})$$


$$1 \text{ F} = 1 \text{ farad} = 1 \text{ C/V} = 1 \text{ coulomb/volt}$$

Parallel-plate capacitor

(a) Arrangement of the capacitor plates

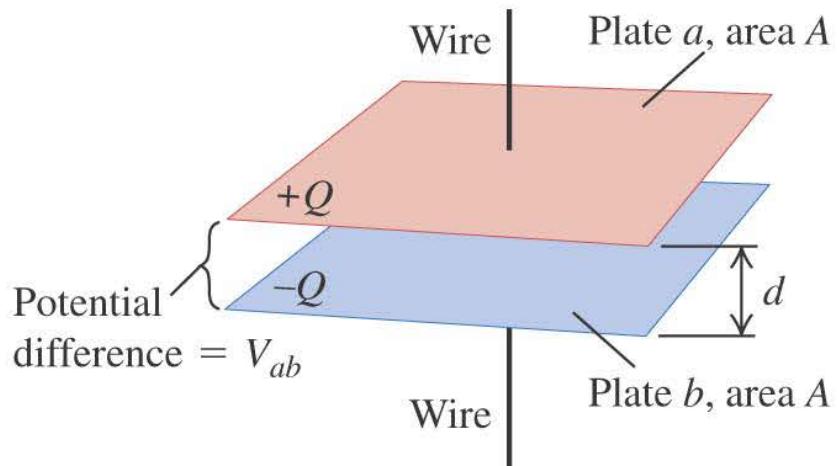

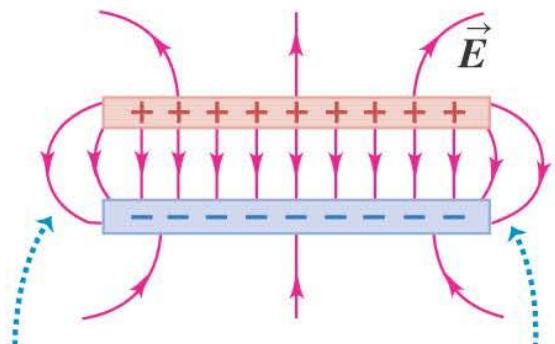
(b) Side view of the electric field \vec{E}




When the separation of the plates is small compared to their size, the fringing of the field is slight.

Parallel-plate capacitor

(a) Arrangement of the capacitor plates

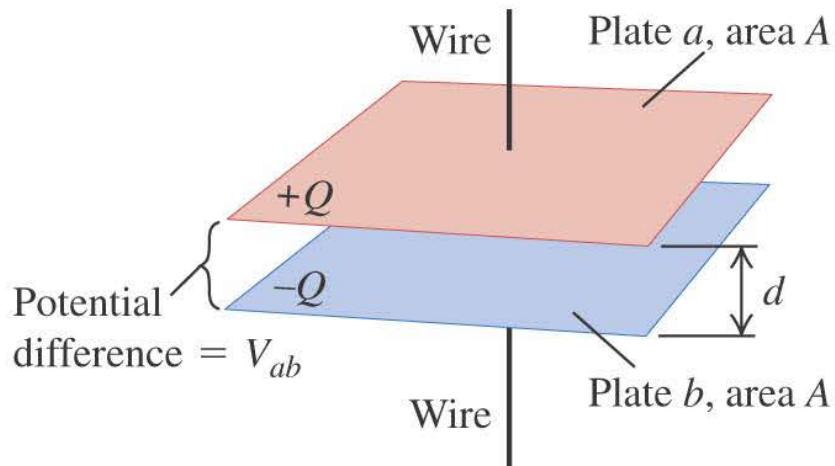

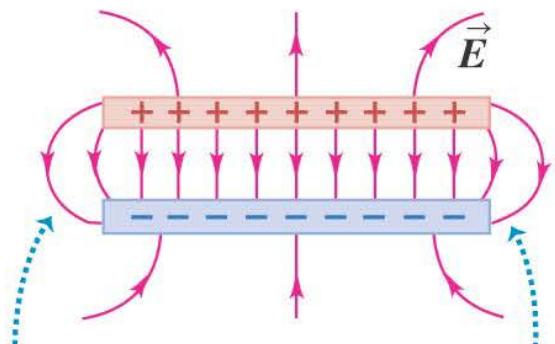(b) Side view of the electric field \vec{E}




When the separation of the plates is small compared to their size, the fringing of the field is slight.

A *parallel-plate capacitor* consists of two parallel conducting plates separated by a distance that is small compared to their dimensions.


The capacitance of a parallel-plate capacitor is $C = \epsilon_0 A/d$

Parallel-plate capacitor

(a) Arrangement of the capacitor plates

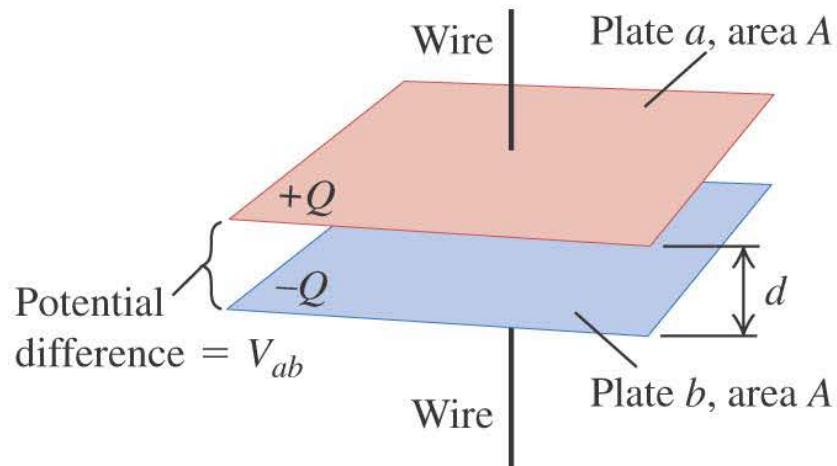

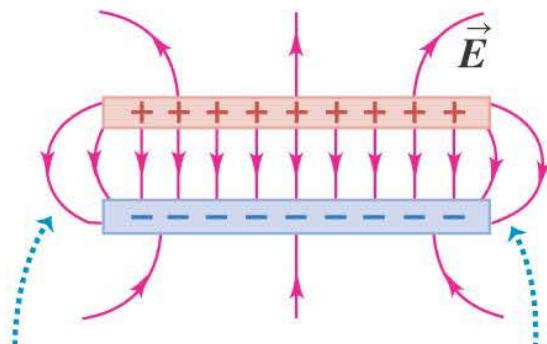(b) Side view of the electric field \vec{E}



When the separation of the plates is small compared to their size, the fringing of the field is slight.


A *parallel-plate capacitor* consists of two parallel conducting plates separated by a distance that is small compared to their dimensions.

The capacitance of a parallel-plate capacitor is $C = \epsilon_0 A/d$


using Gauss's law we found that $E = \sigma/\epsilon_0$ where σ is the magnitude of the surface charge density on each plate. This is equal to the magnitude of the total charge Q on each plate divided by the area A of the plate, or $\sigma = Q/A$, so the field magnitude E can be expressed as

Parallel-plate capacitor

(a) Arrangement of the capacitor plates

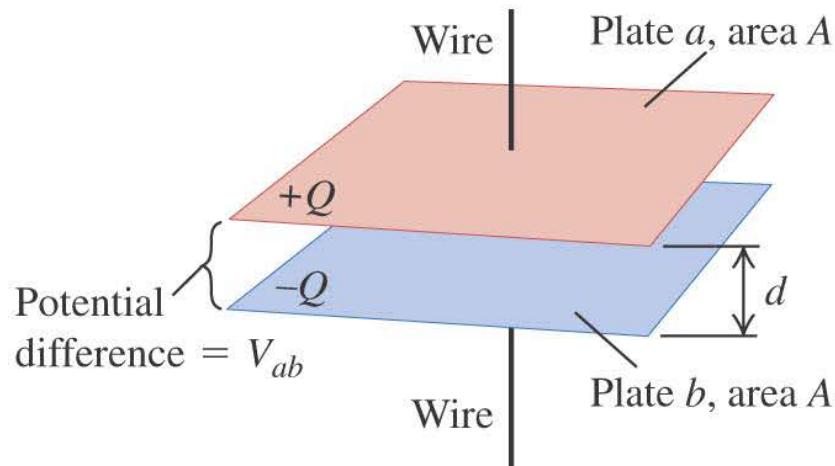

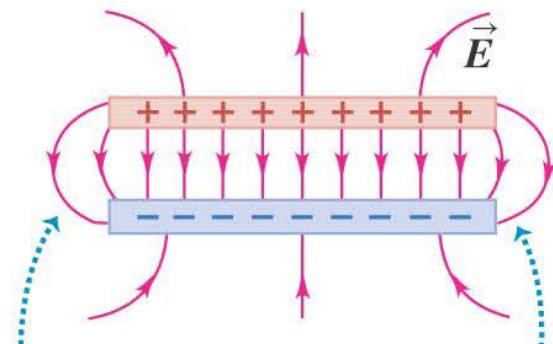(b) Side view of the electric field \vec{E}



When the separation of the plates is small compared to their size, the fringing of the field is slight.

A parallel-plate capacitor consists of two parallel conducting plates separated by a distance that is small compared to their dimensions.

The capacitance of a parallel-plate capacitor is $C = \epsilon_0 A/d$

using Gauss's law we found that $E = \sigma/\epsilon_0$ where σ is the magnitude of the surface charge density on each plate. This is equal to the magnitude of the total charge Q on each plate divided by the area A of the plate, or $\sigma = Q/A$, so the field magnitude E can be expressed as


$$E = \frac{\sigma}{\epsilon_0} = \frac{Q}{\epsilon_0 A} \quad \rightarrow \quad V_{ab} = Ed = \frac{1}{\epsilon_0} \frac{Qd}{A}$$

$$C = \frac{Q}{V_{ab}} = \epsilon_0 \frac{A}{d} \quad (\text{capacitance of a parallel-plate capacitor in vacuum})$$

$$1 \text{ F} = 1 \text{ C}^2/\text{N} \cdot \text{m} = 1 \text{ C}^2/\text{J}$$

$$\epsilon_0 = 8.85 \times 10^{-12} \text{ F/m}$$

Spherical capacitor

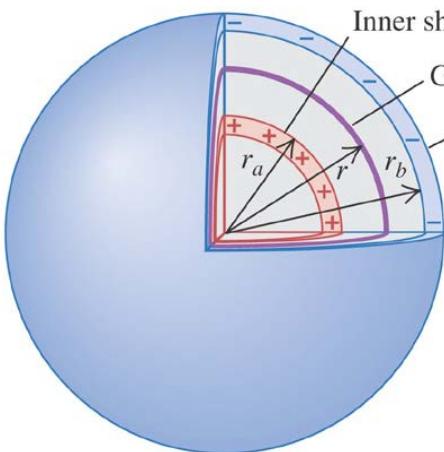


$$\oint \vec{E} \cdot d\vec{A} = \frac{Q_{\text{encl}}}{\epsilon_0} \rightarrow (E)(4\pi r^2) = \frac{Q}{\epsilon_0} \rightarrow E = \frac{Q}{4\pi\epsilon_0 r^2}$$

$$V_{ab} = V_a - V_b = \frac{Q}{4\pi\epsilon_0 r_a} - \frac{Q}{4\pi\epsilon_0 r_b} = \frac{Q}{4\pi\epsilon_0} \left(\frac{1}{r_a} - \frac{1}{r_b} \right) = \frac{Q}{4\pi\epsilon_0} \frac{r_b - r_a}{r_a r_b}$$

$$\rightarrow C = \frac{Q}{V_{ab}} = 4\pi\epsilon_0 \frac{r_a r_b}{r_b - r_a}$$

Spherical capacitor

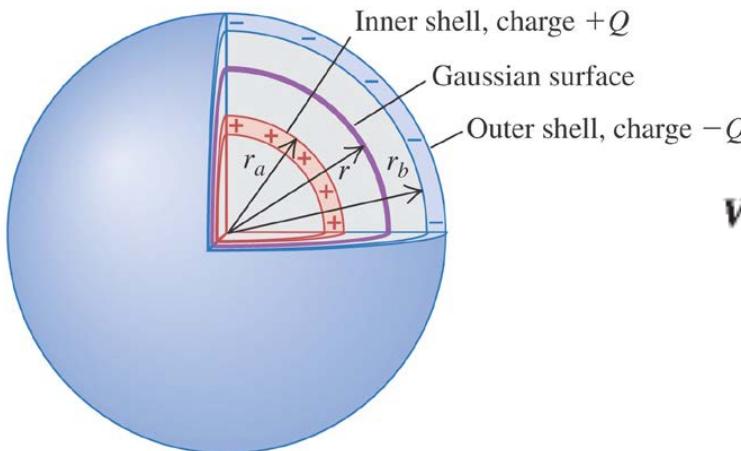


$$\oint \vec{E} \cdot d\vec{A} = \frac{Q_{\text{encl}}}{\epsilon_0} \rightarrow (E)(4\pi r^2) = \frac{Q}{\epsilon_0} \rightarrow E = \frac{Q}{4\pi\epsilon_0 r^2}$$

$$V_{ab} = V_a - V_b = \frac{Q}{4\pi\epsilon_0 r_a} - \frac{Q}{4\pi\epsilon_0 r_b} = \frac{Q}{4\pi\epsilon_0} \left(\frac{1}{r_a} - \frac{1}{r_b} \right) = \frac{Q}{4\pi\epsilon_0} \frac{r_b - r_a}{r_a r_b}$$


$$\rightarrow C = \frac{Q}{V_{ab}} = 4\pi\epsilon_0 \frac{r_a r_b}{r_b - r_a}$$

A cylindrical capacitor

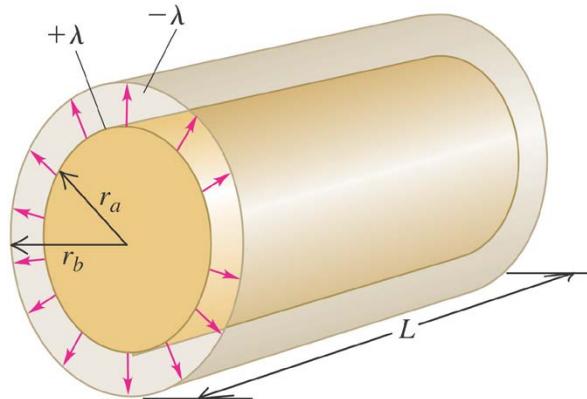

$$V = \frac{\lambda}{2\pi\epsilon_0} \ln \frac{r_0}{r} \rightarrow V_{ab} = \frac{\lambda}{2\pi\epsilon_0} \ln \frac{r_b}{r_a}$$

Spherical capacitor

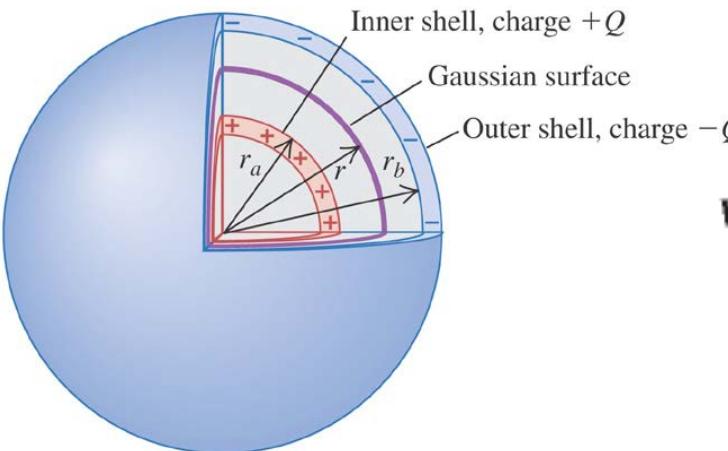


$$\oint \vec{E} \cdot d\vec{A} = \frac{Q_{\text{encl}}}{\epsilon_0} \rightarrow (E)(4\pi r^2) = \frac{Q}{\epsilon_0} \rightarrow E = \frac{Q}{4\pi\epsilon_0 r^2}$$

$$V_{ab} = V_a - V_b = \frac{Q}{4\pi\epsilon_0 r_a} - \frac{Q}{4\pi\epsilon_0 r_b} = \frac{Q}{4\pi\epsilon_0} \left(\frac{1}{r_a} - \frac{1}{r_b} \right) = \frac{Q}{4\pi\epsilon_0} \frac{r_b - r_a}{r_a r_b}$$

$$\rightarrow C = \frac{Q}{V_{ab}} = 4\pi\epsilon_0 \frac{r_a r_b}{r_b - r_a}$$

A cylindrical capacitor

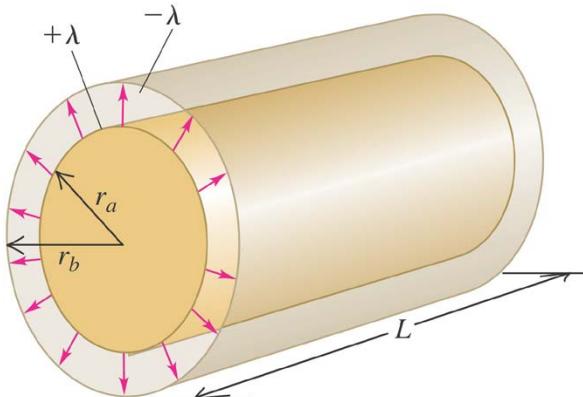

$$V = \frac{\lambda}{2\pi\epsilon_0} \ln \frac{r_0}{r} \rightarrow V_{ab} = \frac{\lambda}{2\pi\epsilon_0} \ln \frac{r_b}{r_a}$$

$$C = \frac{Q}{V_{ab}} = \frac{\lambda L}{\frac{\lambda}{2\pi\epsilon_0} \ln \frac{r_b}{r_a}} = \frac{2\pi\epsilon_0 L}{\ln(r_b/r_a)}$$

$$\rightarrow \frac{C}{L} = \frac{2\pi\epsilon_0}{\ln(r_b/r_a)}$$


Capacitors in series

(a) Two capacitors in series


Capacitors in series:

- The capacitors have the same charge Q .
- Their potential differences add:

$$V_{ac} + V_{cb} = V_{ab}.$$

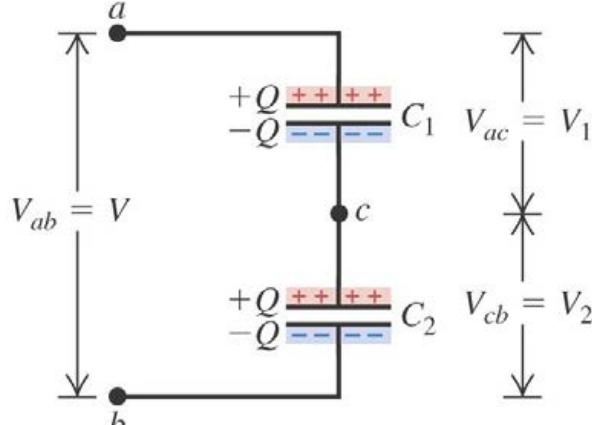

(b) The equivalent single capacitor

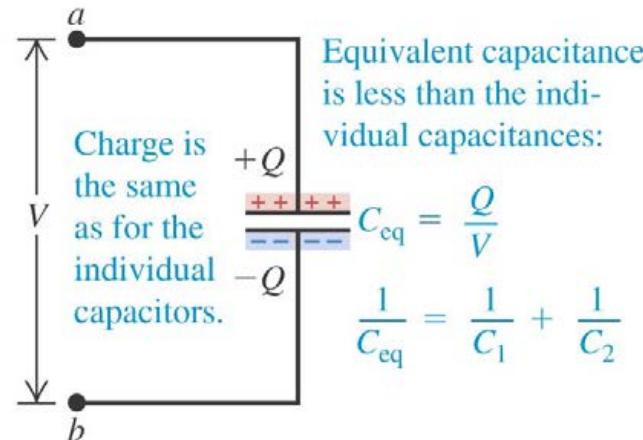


Capacitors in series

(a) Two capacitors in series

Capacitors in series:


- The capacitors have the same charge Q .
- Their potential differences add:

$$V_{ac} + V_{cb} = V_{ab}.$$

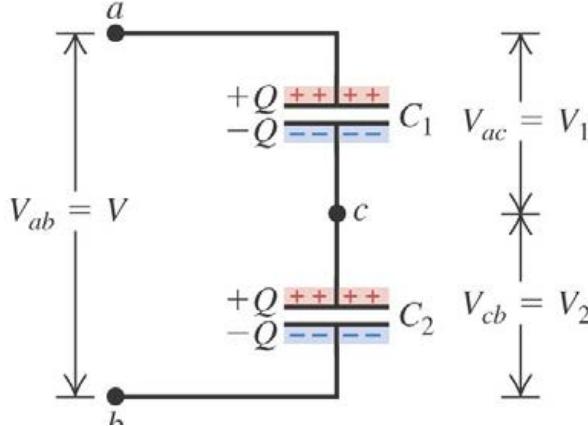

$$V_{ac} = V_1 = \frac{Q}{C_1} \quad V_{cb} = V_2 = \frac{Q}{C_2} \quad \rightarrow \quad V_{ab} = V = V_1 + V_2 = Q \left(\frac{1}{C_1} + \frac{1}{C_2} \right)$$

(b) The equivalent single capacitor

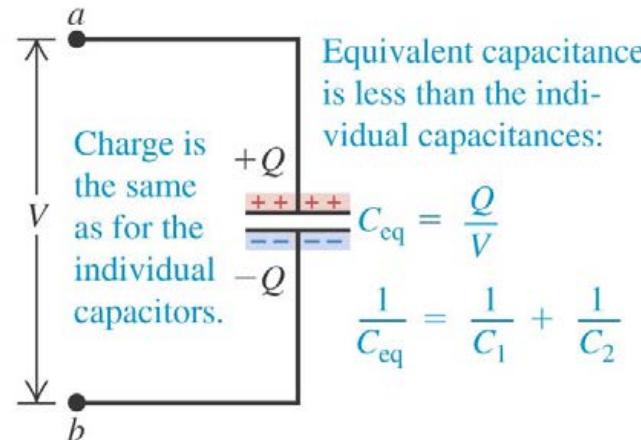

$$\frac{V}{Q} = \frac{1}{C_1} + \frac{1}{C_2} \quad \rightarrow$$

$$\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots \quad (\text{capacitors in series})$$


Capacitors in parallel

Capacitors are connected in *parallel* between *a* and *b* if the potential difference V_{ab} is the same for all the capacitors.

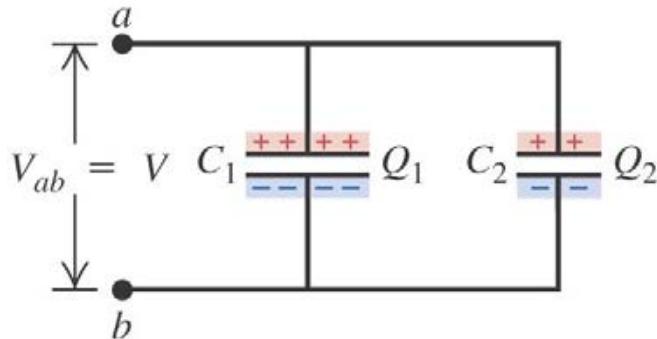
(a) Two capacitors in parallel

Capacitors in parallel:

- The capacitors have the same potential V .
- The charge on each capacitor depends on its capacitance: $Q_1 = C_1 V$, $Q_2 = C_2 V$.



(b) The equivalent single capacitor

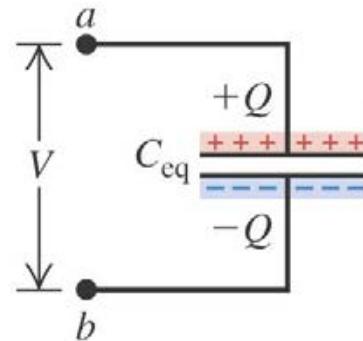

Charge is the sum of the individual charges:

$$Q = Q_1 + Q_2$$

Equivalent capacitance:

$$C_{\text{eq}} = C_1 + C_2$$


Capacitors in parallel

Capacitors are connected in *parallel* between *a* and *b* if the potential difference V_{ab} is the same for all the capacitors.

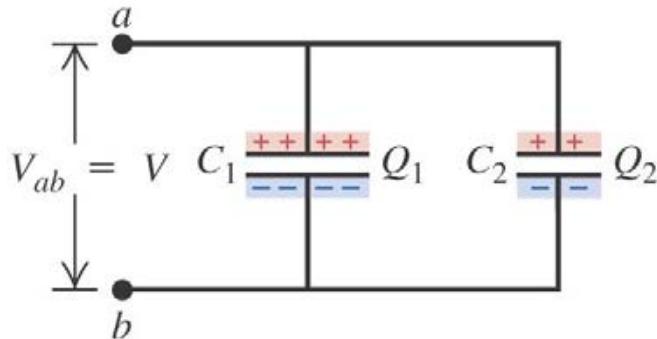
(a) Two capacitors in parallel

Capacitors in parallel:

- The capacitors have the same potential V .
- The charge on each capacitor depends on its capacitance: $Q_1 = C_1 V$, $Q_2 = C_2 V$.



(b) The equivalent single capacitor

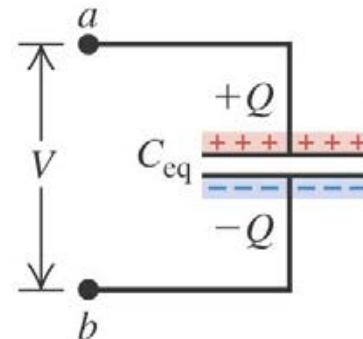

Charge is the sum of the individual charges:

$$Q = Q_1 + Q_2$$


Equivalent capacitance:
 $C_{\text{eq}} = C_1 + C_2$

$$Q_1 = C_1 V \quad \text{and} \quad Q_2 = C_2 V \quad \rightarrow \quad Q = Q_1 + Q_2 = (C_1 + C_2)V$$

→ $\frac{Q}{V} = C_1 + C_2 \quad \rightarrow \quad C_{\text{eq}} = C_1 + C_2$

$C_{\text{eq}} = C_1 + C_2 + C_3 + \dots$ (capacitors in parallel)

Calculations of capacitance

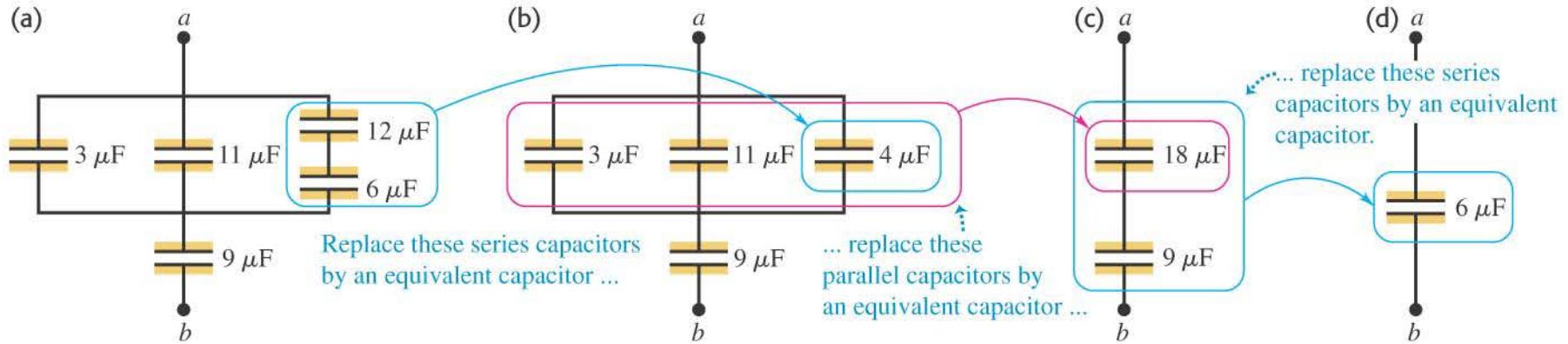

These capacitors are neither all in series nor all in parallel. We can, however, identify portions of the arrangement that *are* either in series or parallel.

We first replace the 12- μF and 6- μF series combination by its equivalent capacitance C'

$$\frac{1}{C'} = \frac{1}{12 \mu\text{F}} + \frac{1}{6 \mu\text{F}} \quad C' = 4 \mu\text{F}$$

Now we see three capacitors in parallel, and we replace them with their equivalent capacitance C''

$$C'' = 3 \mu\text{F} + 11 \mu\text{F} + 4 \mu\text{F} = 18 \mu\text{F}$$

→

$$\frac{1}{C_{\text{eq}}} = \frac{1}{18 \mu\text{F}} + \frac{1}{9 \mu\text{F}} \quad C_{\text{eq}} = 6 \mu\text{F}$$

Energy stored in a capacitor

- The electric potential energy stored in a charged capacitor is just equal to the amount of work required to charge it.
- When the capacitor is dis- charged, this stored energy is recovered as work done by electrical forces.
- We can calculate the potential energy U of a charged capacitor by calculating the work W required to charge it. Suppose that when we are done charging the capacitor, the final charge is Q and the final potential difference is V .

$$V = \frac{Q}{C}$$

Energy stored in a capacitor

- The electric potential energy stored in a charged capacitor is just equal to the amount of work required to charge it.
- When the capacitor is dis- charged, this stored energy is recovered as work done by electrical forces.
- We can calculate the potential energy U of a charged capacitor by calculating the work W required to charge it. Suppose that when we are done charging the capacitor, the final charge is Q and the final potential difference is V .

$$V = \frac{Q}{C}$$

Let q and v be the charge and potential difference, respectively, at an intermediate stage during the charging process; then $v = q/C$. At this stage the work dW required to transfer an additional element of charge dq is

$$dW = v dq = \frac{q dq}{C}$$

Energy stored in a capacitor

- The electric potential energy stored in a charged capacitor is just equal to the amount of work required to charge it.
- When the capacitor is dis- charged, this stored energy is recovered as work done by electrical forces.
- We can calculate the potential energy U of a charged capacitor by calculating the work W required to charge it. Suppose that when we are done charging the capacitor, the final charge is Q and the final potential difference is V .

$$V = \frac{Q}{C}$$

Let q and v be the charge and potential difference, respectively, at an intermediate stage during the charging process; then $v = q/C$. At this stage the work dW required to transfer an additional element of charge dq is

$$dW = v dq = \frac{q dq}{C} \quad \rightarrow \quad W = \int_0^W dW = \frac{1}{C} \int_0^Q q dq = \frac{Q^2}{2C} \quad (\text{work to charge a capacitor})$$

Energy stored in a capacitor

- The electric potential energy stored in a charged capacitor is just equal to the amount of work required to charge it.
- When the capacitor is dis- charged, this stored energy is recovered as work done by electrical forces.
- We can calculate the potential energy U of a charged capacitor by calculating the work W required to charge it. Suppose that when we are done charging the capacitor, the final charge is Q and the final potential difference is V .

$$V = \frac{Q}{C}$$

Let q and v be the charge and potential difference, respectively, at an intermediate stage during the charging process; then $v = q/C$. At this stage the work dW required to transfer an additional element of charge dq is

$$dW = v dq = \frac{q dq}{C} \quad \rightarrow \quad W = \int_0^W dW = \frac{1}{C} \int_0^Q q dq = \frac{Q^2}{2C} \quad (\text{work to charge a capacitor})$$

$$U = \frac{Q^2}{2C} = \frac{1}{2} CV^2 = \frac{1}{2} QV \quad (\text{potential energy stored in a capacitor})$$

Energy stored in a capacitor

- The electric potential energy stored in a charged capacitor is just equal to the amount of work required to charge it.
- When the capacitor is dis- charged, this stored energy is recovered as work done by electrical forces.
- We can calculate the potential energy U of a charged capacitor by calculating the work W required to charge it. Suppose that when we are done charging the capacitor, the final charge is Q and the final potential difference is V .

$$V = \frac{Q}{C}$$

Let q and v be the charge and potential difference, respectively, at an intermediate stage during the charging process; then $v = q/C$. At this stage the work dW required to transfer an additional element of charge dq is

$$dW = v dq = \frac{q dq}{C} \quad \rightarrow \quad W = \int_0^W dW = \frac{1}{C} \int_0^Q q dq = \frac{Q^2}{2C} \quad (\text{work to charge a capacitor})$$

$$U = \frac{Q^2}{2C} = \frac{1}{2}CV^2 = \frac{1}{2}QV \quad (\text{potential energy stored in a capacitor})$$


Electric-Field Energy

$$u = \text{Energy density} = \frac{\frac{1}{2}CV^2}{Ad} \quad \rightarrow$$

$$u = \frac{1}{2}\epsilon_0 E^2 \quad (\text{electric energy density in a vacuum})$$


Some examples of capacitor energy

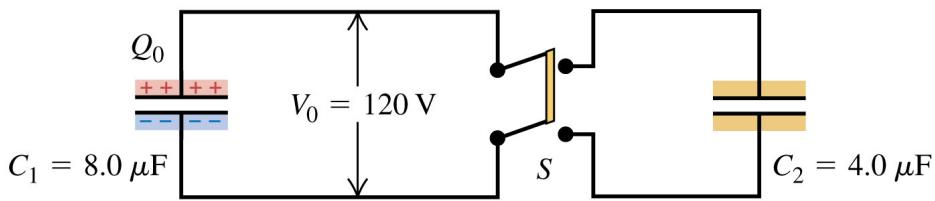We connect a capacitor $C_1 = 8.0 \mu\text{F}$ to a power supply, charge it to a potential difference $V_0 = 120 \text{ V}$, and disconnect the power supply. Switch S is open.



Some examples of capacitor energy

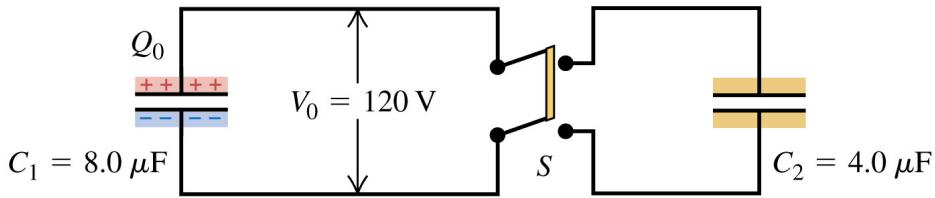
We connect a capacitor $C_1 = 8.0 \mu\text{F}$ to a power supply, charge it to a potential difference $V_0 = 120 \text{ V}$, and disconnect the power supply. Switch S is open.



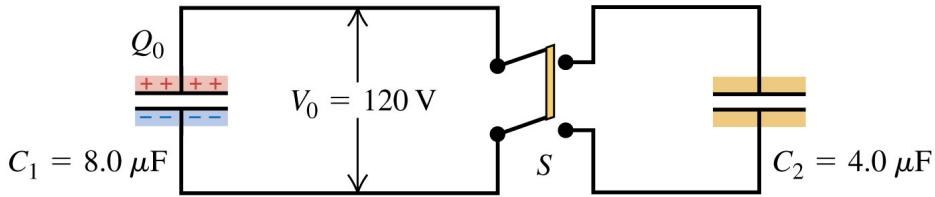- (a) What is the charge Q_0 on C_1 ?
- (b) What is the energy stored in C_1 ?
- (c) Capacitor $C_2 = 4.0 \mu\text{F}$ is initially uncharged. We close switch S . After charge no longer flows, what is the potential difference across each capacitor, and what is the charge on each capacitor?
- (d) What is the final energy of the system?

Some examples of capacitor energy

We connect a capacitor $C_1 = 8.0 \mu\text{F}$ to a power supply, charge it to a potential difference $V_0 = 120 \text{ V}$, and disconnect the power supply. Switch S is open.




- (a) What is the charge Q_0 on C_1 ?
- (b) What is the energy stored in C_1 ?
- (c) Capacitor $C_2 = 4.0 \mu\text{F}$ is initially uncharged. We close switch S . After charge no longer flows, what is the potential difference across each capacitor, and what is the charge on each capacitor?
- (d) What is the final energy of the system?

- (a) The initial charge Q_0 on C_1 is

$$Q_0 = C_1 V_0 = (8.0 \mu\text{F})(120 \text{ V}) = 960 \mu\text{C}$$

Some examples of capacitor energy

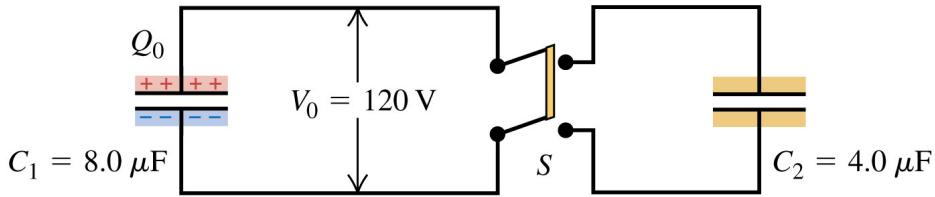We connect a capacitor $C_1 = 8.0 \mu\text{F}$ to a power supply, charge it to a potential difference $V_0 = 120 \text{ V}$, and disconnect the power supply. Switch S is open.



- (a) What is the charge Q_0 on C_1 ?
- (b) What is the energy stored in C_1 ?
- (c) Capacitor $C_2 = 4.0 \mu\text{F}$ is initially uncharged. We close switch S . After charge no longer flows, what is the potential difference across each capacitor, and what is the charge on each capacitor?
- (d) What is the final energy of the system?

- (a) The initial charge Q_0 on C_1 is


$$Q_0 = C_1 V_0 = (8.0 \mu\text{F})(120 \text{ V}) = 960 \mu\text{C}$$

- (b) Energy initially stored

$$U_{\text{initial}} = \frac{1}{2} Q_0 V_0 = \frac{1}{2}(960 \times 10^{-6} \text{ C})(120 \text{ V}) = 0.058 \text{ J}$$

Some examples of capacitor energy

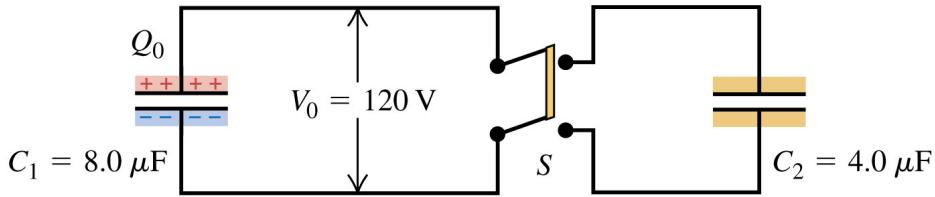We connect a capacitor $C_1 = 8.0 \mu\text{F}$ to a power supply, charge it to a potential difference $V_0 = 120 \text{ V}$, and disconnect the power supply. Switch S is open.



- (a) What is the charge Q_0 on C_1 ?
(b) What is the energy stored in C_1 ?
(c) Capacitor $C_2 = 4.0 \mu\text{F}$ is initially uncharged. We close switch S . After charge no longer flows, what is the potential difference across each capacitor, and what is the charge on each capacitor?
(d) What is the final energy of the system?

- (a) The initial charge Q_0 on C_1 is

$$Q_0 = C_1 V_0 = (8.0 \mu\text{F})(120 \text{ V}) = 960 \mu\text{C}$$

- (b) Energy initially stored

$$U_{\text{initial}} = \frac{1}{2} Q_0 V_0 = \frac{1}{2}(960 \times 10^{-6} \text{ C})(120 \text{ V}) = 0.058 \text{ J}$$

- (c) When we close the switch $\rightarrow Q_0 = Q_1 + Q_2$

$$\rightarrow V = \frac{Q_0}{C_1 + C_2} = \frac{960 \mu\text{C}}{8.0 \mu\text{F} + 4.0 \mu\text{F}} = 80 \text{ V} \quad \rightarrow \quad Q_1 = 640 \mu\text{C} \quad Q_2 = 320 \mu\text{C}$$

- (d) Final energy of the system

$$\begin{aligned} U_{\text{final}} &= \frac{1}{2} Q_1 V + \frac{1}{2} Q_2 V = \frac{1}{2} Q_0 V \\ &= \frac{1}{2} (960 \times 10^{-6} \text{ C})(80 \text{ V}) = 0.038 \text{ J} \end{aligned}$$